


# amateur radio

Vol. 37, No. 2

FEBRUARY, 1969

Published by C.R.C. Publications, Inc.  
Subscription fee paid in a separate bill

PRICE 35 CENTS

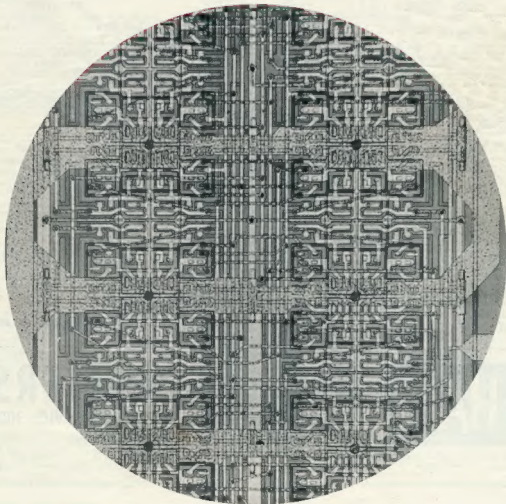

## "KEW" KYORITSU MO 65 METERS

New, Size: 3 1/4 inch, mounting hole 2 1/2 inch.

All plus Postage 20c.

1 mA, 5 mA, 10 mA, 25 mA, 50 mA, 100 mA, 150 mA, 250 mA, 500 mA	\$4.50
1 amp D.C.	\$4.50
5 amp D.C.	\$4.50
10 amp D.C.	\$4.50
30-50 amp D.C.	\$8.25
15v. D.C., 30v. D.C., 300v. D.C.	\$4.50
300 volts A.C.	\$9.50

## CLEAR PLASTIC PANEL METERS

MRP 1 1/4 inch square, clear plastic, 1 inch round mounting hole, 1 1/2 inch deep:

1 milliamperes (mA)	\$3.50
500 microamperes (uA)	\$3.75
5 amperes (A)	\$4.75

Also other types available.

MRP 1 1/4 inch square, clear plastic face, 1 1/2 inch round mounting hole, 1 1/2 inch deep:

50 uA	\$4.00
50-50 uA	\$3.75
1, 5, 10, 20, 50, 100 uA	\$3.75
100-100 uA	\$3.50
500 uA	\$4.00
1 mA	\$3.75
10, 25, 50, 100, 250, 500 mA	\$3.75
1000 volt a.c.	\$4.50

"S" Meter (1 mA f.s.d.) cal. 9-9 (with additional scale in 10 db. steps over 99)

"VU" Meter, scale: minus 20 to plus 3 VU (10 to plus 3 VU in bold red arc). Accuracy: within plus or minus 0.5 db. (at 0 VU)

Stereo Balance Meter (1-10 mA f.s.d.)

Also other types available.

MRP 3 1/4 inch square, clear plastic face, 2 1/4 inch round mounting hole, 1 1/2 inch deep:

50 uA	\$5.00
50-50 uA	\$5.75
100 uA	\$5.75
500 uA	\$5.75
1, 5, 10, 25, 50, 100, 250, and 500 mA	\$5.75

P25 2 1/4 inch square, clear plastic face, 2 1/4 inch round mounting hole, 1 1/2 inch deep:

50 uA	\$5.75
100 uA	\$5.75
500 uA	\$5.75
1, 5, 10, 25, 50, 100, 250, and 500 mA	\$5.75

Postage 25c

## "SPECIAL" CARTRIDGES AND STYLUS

PC3LS Crystal Turnover Mono 1/4 in. mount. \$2.40

Y10 Crystal Stereo Turnover 1/4 in. mount. \$2.50

Y10 Ceramic Stereo Turnover 1/4 in. mount. \$3.50

Mono Ronette 105 Crystal Turnover 1/4 in. mount. \$4.50

Ronette 105 Stereo Diamond Turnover 1/4 in. mount. \$7.00

57A Ceramic Sonotone, 1/2 in. mounting \$6.50

57A Ceramic Diamond, 1/2 in. mounting \$7.00

B.S.R. Type C1, Stereo Ceramic Turnover, 1/2 in. \$7.50

B.S.R. Type TCSM Mono Ceramic Turnover, 1/2 in. \$4.75

B.S.R. Type TCS Stereo Ceramic Turnover, 1/2 in. \$6.50

B.S.R. Type TCS Stereo Ceramic Turnover, 1/2 in. \$6.50

## "NIKKA" 1 WATT TRANSCEIVERS

P.M.G. Approved, Solid State, 14 Transistor Circuit inc. r.f. stage.

27.240 Mc. (provision for two channels).

Range boost circuit.

Up to 10 miles in open country or water.

Buzzer type Call System.

Squish control.

Complete with leather carrying case.

SIXES PAIR

## DISCOUNT SPECIAL BUY BULK AND SAVE New Brand Name Recording Tapes and Accessories

Length	Reel	Reels per Pack	Price
150 ft.	Acetate	3 in.	\$1.75
225 ft.	Acetate	3 in.	\$1.75
300 ft.	Mylar	3 in.	\$1.75
600 ft.	Acetate	5 in.	\$2.25
900 ft.	Acetate	5 in.	\$2.25
1200 ft.	Acetate	7 in.	\$2.50
1800 ft.	Acetate	7 in.	\$2.50
1800 ft.	Mylar	7 in.	\$2.50
2400 ft.	Mylar	7 in.	\$2.50
3600 ft.	Mylar	7 in.	\$13.50

## Tape Accessories

Head Alignment Tape, 100 ft. on 2 1/2 in. reel	\$1.50
Take Clips, packet of 75	\$1.25
Book "Tape Editing and Splicing"	\$5.00
Head Holders, pair	\$1.50
Tape Jockey Cloths, packet of three	\$1.50
Head-Kleen Tape, 225 ft. on 3 in. Reel	\$1.75
"Tape-Clean" Cloth Tape, 3 in. Reel	\$1.75
Head and Guide Cleaner and Lubric Oil	\$1.50
Address Cards, two-sided, packet of 30	\$1.40
Replacement Pressure Pad Kit	\$1.50
Sanding and Coing Patches, Aluminum, packet of 50	\$1.50
Splicing Tape, 1/4 in. wide, 300 in.	\$1.00
Coloured Leader Tape, 5 in. x 2 1/2 in. Reels, 100 ft.	\$4.50
Available separately, all colours per reel	\$1.00
Splicing Tape, 1/4 in. x 100 in.	\$1.00
Head Cleaner	\$1.50
Head and Guide Lubricant	\$1.50
Recorder and Phono Drive Oil	75c
Non-Slip for Tape and Phono Drives	\$1.00

## Phono Accessories

Three Hi-Fi Stereo Record Cleaning Cloths	\$1.15
Record Jockey Cloth	75c
Record Cleaning Kit	\$2.50
Stylus Microscope	\$1.50
Gauge Stylus Pressure	\$1.50

## REPLACEMENT STYLUS AT BARGAIN PRICES

S3/ST Stereo (S325SR) Sapphire, Suit most Japanese Portable Record Players (forked fitting).

Normal Price \$1.35, Special 75c.

NY/ST Stereo (S44SR) Sapphire, Suit Ronette 105.

Normal Price \$1.35, Special 75c.

D8/ST Stereo Diamond (D84SR), Suit Ronette 105.

Normal Price \$5, Special \$3.25.

D51/3S Stereo Diamond (D51SR), Suit B.S.R.

TCS/S, etc. Normal Price \$5, Special \$3.25.

D108/80 Stereo Diamond (D08SR) L.P. Stereo/78.

Suit B.S.R. C1, etc. Normal Price \$7, Special \$4.75.

D258 Stereo Diamond (D25SR) L.P. Stereo/78.

Suit Dual DNS, D05830, Normal Price \$7, Special \$4.75.

## MULTIMETER—Model OL64

20,000 ohms per volt D.C., 8,000 ohms per volt A.C.

D.C. Voltage: 0-0.3, 1, 10, 30, 250, 500, 1,000, 5,000.

A.C. Voltage: 0-10, 30, 250, 500, 1,000.

D.C. Current: 0-30 uA, 1, 50, 500 mA, 10 A.

Resistance: 0-5, 500K ohms, 550M ohms.

Decibels: minus 20 to plus 22 db., plus 20 to plus 40 db.

Capacitance: 250 pF. to 0.02 uF.

Inductance: 0-500 H.

Load Current: 0-0.05, 0.5, 50, 80 mA.

Self contained Batteries: 22.5v. (8L015) x 1; 1.5v.

(UM3) x 2.

Size and Weight: 6 in. x 4-1/2 in. x 2 in.; 850 g.

Meter Movement Fundamental Sensitivity: 30 uA.

F.S.D.

Meter Movement Internal Resistance: 3,100 ohm

plus or minus 3 per cent.

Allowance:

For D.C. Voltage range, plus or minus 3 per cent. of specified value.

For D.C. Current range, plus or minus 3 per cent. of specified value.

For A.C. Voltage range, plus or minus 4 per cent. of specified value.

For Resistance range, plus or minus 3 per cent. of scale length.

For Decibel range, plus or minus 4 per cent. of specified value.

PRICE: \$19.75

## TRIO COMMUNICATIONS RECEIVERS

Trio Model 9RS9DE, four bands covering 540 Kc. to 30 Mc., two mechanical filters for maximum selectivity. Product Detector for S.S.S. reception.

Large tuning and bandspread dial for accurate tuning. Automatic noise limiter, calibrated electrical bandspread, 8 sections and S.F.O. 2 micro-volt sensitivity for 10 db. S/N ratio.

PRICE \$175

TRADE-IN ACCEPTED

## MAGNETIC CARTRIDGES

CM503 Magnetic Stereo Diamond, 4 mV, at 1 Kc., 20-20,000 c/s., 3 grams tracking weight.

Spere Stylus \$4.25

MC/Magnetic Stereo, 0.7 mV, Diamond, 8 mV, at 1 Kc., 20-21,000 c/s., 2 grams tracking weight.

Spere Stylus \$5.50

Spere Stylus \$5.50

Spere Stylus \$5.50

Spere Stylus \$5.50

# RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-5286 All Mail to be addressed to above address

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc.

# amateur radio

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA      FOUNDED 1910



FEBRUARY 1969

Vol. 37, No. 2

## Publishers:

VICTORIAN DIVISION W.I.A.  
Reg. Office: 478 Victoria Parade, East Melbourne, Vic., 3002.

## Editor:

K. E. PINCOTT ..... VK3AFJ

## Assistant Editor:

E. C. Manifold ..... VK3EM

## Publications Committee:

G. W. Bely (Secretary) ..... VK3AOM  
A. W. Chandler (Circulation) ..... VK3LSC  
Ken Gillespie ..... VK3GK

## Draughtsmen:

Clem Allan ..... VK3ZIV  
Peter Ramsay ..... VK3ZWN  
Ian Smith ..... 36 Green St., Noble Park

## Advertising Enquiries:

C/o, P.O. Box 36, East Melbourne, Vic., 3002.  
or  
Mrs. BELLARS, Phone 41-3535, 478 Victoria  
Parade, East Melbourne, Vic., 3002. Hours:  
10 a.m. to 3 p.m. only.

Advertising copy (except Hamads) should be  
forwarded direct to the printers by first of  
each month.

## Printers:

"RICHMOND CHRONICLE," Phone 42-2419.  
Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than  
subscriptions, should be addressed to:

THE EDITOR,  
"AMATEUR RADIO,"  
P.O. BOX 36,  
EAST MELBOURNE, VIC., 3002.



Members of the W.I.A. should refer all enquiries  
regarding delivery of "A.R." direct to their  
Divisional Secretary and not to "A.R." direct.  
Non-members of the W.I.A. should write to the  
Victorian Division, C/o, P.O. Box 36, East  
Melbourne. Two months' notice is required  
before a change of mailing address can be  
effected. Readers should note that any change  
in the address of their transmitting station  
must, by P.M.G. regulation, be notified to the  
P.M.G. in the State of residence; in addition,  
"A.R." should also be notified. A convenient  
form is provided in the "Call Book".



Direct subscription rate is \$3.60 a year, post  
paid, in advance. Single copies 30c. Issued  
monthly on first of the month. February edition  
excepted.

## CONTENTS

### Technical Articles:—

	Page
Locally Available VHF Field Effect Transistors .....	15
Project—Solid State Transceiver, Part Four .....	13
Putting the Geloso G222 on 160 Metres .....	11
Solid State Coupling Methods .....	9
VK3 VHF Group Two Metre Converter .....	6

### General:—

Amateur Radio and the 1968 Blue Mountains Bushfires .....	17
Correspondence .....	21
DX .....	20
Fairchild Wins Top Award .....	8
Federal QSL Bureau .....	21
New Call Signs .....	18
Painton Technical Data .....	21
Prediction Charts for February 1969 .....	22
Silent Keys .....	21
The Questionnaire—A Progress Report .....	19
W.I.A. DXCC .....	12

### Contests:—

Australian Results of 34th A.R.R.L. DX Competition .....	16
Australian Results of 1968 WPX SSB Contest .....	16
B.A.R.T.G. Spring RTTY Contest .....	16
Contest Calendar .....	19

## Cover Story

Our front cover this month depicts  
portion of a recently introduced inte-  
gration system developed by Fairchild,  
known as the 4500 "Micromatrix".  
Designed for large and medium scale  
integration, the 4500 "Micromatrix" is  
the first in a series of cellular arrays.  
It consists of an array of eight identi-  
cal cells arranged by a 4 x 2 pattern.  
Each cell contains four 4-input DTL  
NAND gates; interconnection of the  
gates is performed with a two-layer  
metalisation to meet various require-  
ments. More about "Micromatrix"  
elsewhere this issue.



## DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

### GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,  
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)  
Telegram: "Metals," Melb.



HANSON ROAD,  
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)  
Telegrams: "Metals," Adel.

## CALL BOOK

1968-69 EDITION

NOW AVAILABLE!

75 Cents, from your usual Supplier

## BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY  
AND OUTPUT



Our Crystals cover all types and frequencies in common use and include overtones, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:

6280, 4095, 4535, 2760, 2524 Kc.  
5,500 Kc. T.V. Sweep Generator Crystals, \$7.25;  
100 Kc. and 1000 Kc. Frequency Standard, \$17;  
plus Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, \$13 each plus Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 Mc. AND 7 Mc. BAND.

Commercial—0.02% \$7.25, 0.01% \$7.55, plus Sales Tax.

Amateur—from \$6 each, plus Sales Tax.

Regrinds—Amateur \$3, Commercial \$3.75.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carrell, Box 2102, Auckland.  
Contractors to Federal and State Government Departments.

### BRIGHT STAR RADIO

LOT 6, EILEEN ROAD, CLAYTON, VIC.

Phone 546-5076

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



A PUBLICATION FOR THE RADIO AMATEUR  
Look for it on every radio shop and electronic store

VHF COMMUNICATIONS, the International Edition, printed in English, of the well established German Publication UKW-BERICHT, is an Amateur Radio magazine catering especially for the VHF, UHF and Microwave enthusiast.

VHF COMMUNICATIONS will follow the same path as UKW-BERICHT, by specialising in the publication of exact and extensive assembly instructions for VHF, UHF and Microwave transmitters, receivers, converters, transceivers, antennas, measuring equipment and accessories, which can be easily duplicated. The latest advances in semiconductors, printed circuits and electronic technology are described in great detail. For most articles, all the special components required for the assembly of the described equipment, such as epoxy printed circuit boards, trimmers, coil formers, as well as metal parts and complete kits will be available from the Australasian Representative.

VHF COMMUNICATIONS also features information regarding the development of electronic equipment, measuring methods, as well as technical reports covering new techniques, new components and new equipment for the Amateur.

VHF COMMUNICATIONS is a quarterly, published in February, May, August and November. Each edition contains roughly sixty pages of technical information and articles.

VHF COMMUNICATIONS' subscription rate (air mailed direct from the publisher) is \$5.50 per year. Every copy is dispatched in a sealed envelope to ensure that it arrives in perfect condition.

Some copies of the German edition UKW-Berichte are available free for perusal. Subscriptions, either cheque or money order/postal note should be forwarded to the Australasian Representative, Mr. Gordon Clarke, 2 Beaconview St., Belgoviah, N.S.W., 2093, Australia.



ZEITSCHRIFT FÜR DEN VHF-UHF-AMATEUR  
GERÄTEANLEITUNGEN UND THEORETISCHE TECHNISCHE

## VHF-UHF OSCILLATORS

Presented below, for readers of Amateur Radio is a list of Fairchild Semiconductor devices and circuit diagrams for use in the construction of VHF and UHF oscillators. At the foot of the page there are brief specifications for the recommended devices taken from the Fairchild Short Form Catalogue.

**2N915-6**

**NPN Silicon Planar Transistors designed specifically for Low Noise VHF Amplifier and Oscillator applications.**

## 2N918

**NPN Silicon Planar Transistor for use in 1 K MHz Oscillator Circuits with rise and fall time of less than 2.5 nSecs.**

**SE1001-2**

NPN Silicon Planar Transistors designed for use in **high power gain**, VHF Amplifier and Oscillator Circuits.

## SE1010

NPN Silicon Planar Transistor designed specifically as **Low Noise** VHF Amplifier and Oscillator.

## SE3001-2

**NPN Silicon Planar Transistors for use in UHF Oscillator Circuit applications, featuring high power gain, low leakage and typical  $f_T$  of 900 MHz.**

## SE5022



**NPN Silicon Planar Transistor** designed for use as VHF Oscillator and Amplifier, featuring **high power gain at 200 MHz.**

## AY7101

NPN Silicon Planar Transistor designed for **wide band** RF application and VHF Oscillator application.

**AY7104**

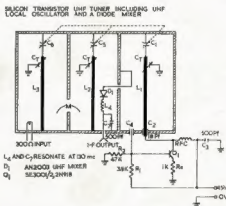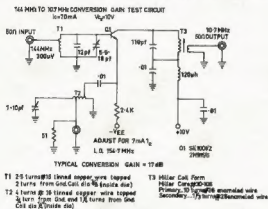**NPN Silicon Planar Transistor for use in Low Power non-saturating switching circuits and VHF Amplifier and Oscillator Circuits.**



ELECTRICAL CHARACTERISTICS @ 25°C.

TYPE No.	LVCEO @ ICmA Volts. min.	hFE min.-max. @ ICmA/VCE Volts.	VCE (sat.) @ ICmA/IBmA Volts. max.	ICBO @ VCB nA	fT min. MHz	Pwr. Total @ 25°C Free Air mW
2N915	50 @ 10	50 @ 10/5	1 @ 10/1	10 @ 60	250	360
2N916	25 @ 10	50 @ 10/1	0.5 @ 10/1	10 @ 30	300	360
2N918	15 @ 3	20 @ 3/1	0.4 @ 10/1	10 @ 15	600	200
SE1001	45 @ 10	40 @ 10/10	2.0 @ 10/1	500 @ 30	200	200
SE1002	45 @ 10	100 @ 10/10	2.0 @ 10/1	500 @ 30	200	200
SE1010	15 @ 10	20 @ 2/10	0.3 @ 10/1	500 @ 15	200	250
SE3001	12 @ 3	20 @ 8/10	0.6 @ 10/1	500 @ 15	600	200
SE3002	12 @ 3	20 @ 8/10	0.6 @ 10/1	500 @ 15	600	200
SE5022	20 @ 1	20-200 @ 4/5	3 @ 10/5	50 @ 10	300	175
AY7101	15 @ 10	20 @ 2/10	0.3 @ 20/2	50 @ 15	400	300
AY7104	45 @ 10	40 @ 10/10	1.2 @ 10/1	50 @ 35	250	300

For further information, data sheets and application bulletins, write or phone the Marketing Services Department, Fairchild Australia Pty. Ltd. Prices on application.

**FAIRCHILD**  
AUSTRALIA PTY. LTD.

420 MT, DANDENONG ROAD, CROYDON, 3136.

1992



## ... Going SSB?

**BAIL ELECTRONIC SERVICES** have the answers!  
**Widest choice from the YAESU Australian Agents.**

**FRDX-400 Receiver:** 160-10 mx, I.F. "T" notch filter, 100/25 Kc. calibrator, selectable slow/fast AGC, provision for internal installation of FET VHF converters, FM with squelch. Laboratory proven, outstanding sensitivity. Can be linked with FLDX-400 for transceiving.

**FLDX-400 Transmitter:** PA 2 x 6JS6A, 300w. speech peak input. Mechanical filter, VOX, ALC; adaptable to FSK for RTTY.

**FTDX-400 Transceiver:** 80/10 mx, 400-500w., built-in AC power supply, VOX, ALC, off-set tuning, calibrator . . . the lot!

**Also available:** Transceiver FT-50, Transmitter FL-50, Receiver FR-50, Low Pass Filter FF-30DX, Type "F" SSB Generator Assembly, SWR Meter K-109, Yaesu valves and spares, Co-ax. Connectors, Hy-Gain [U.S.A.] Beams.

**BAIL POLICY:** Manufacturer-backed 90-day warranty. All sets are tested before despatch. After-sales service and spares availability.

Full details from the authorised Australian Agent:

**BAIL ELECTRONIC SERVICES**, 60 Shannon St., Box Hill North, Vic., 3129. Ph. 89-2213

Rep. in N.S.W.: A. J. ("SANDY") BRUCE SMITH, 47 Hyman Street, Tamworth, N.S.W., 2340. Telephone (STD 067) 66-1010

# dynamic!



**TRIMAX**  
**extended range**  
**volume indicator**

The Trimax G54 Solid State Volume Indicator has been specifically designed for dynamic programme level measurements, with a meter having the fast rise time required to detect the peaks of programme material. Its application, however, extends to the entire field of level measurement in the audio frequency range. The accuracy of calibration and small attenuator increments (2 db steps) also make it particularly suitable for the lining up and transmission testing of an entire system.

A high-quality shielded input transformer enables the instrument to be used on balanced or unbalanced systems.

**L M Ericsson Pty. Ltd.**  
**TRIMAX DIVISION**

Cnr. Charles Street and Williams Rd,  
 North Coburg 3058, Vic., Aust.  
 Phone 35 1203.  
 Cables and telegrams:  
 Trimax, Melbourne.



# Painton Reliability and Quality


## CONNECTORS

A range from 2 contacts to 71 contacts which will meet most requirements.



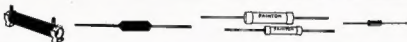
## RESISTORS

An almost infinite variety in wire-wound, cracked carbon and metal film.



## FADERS ATTENUATORS SWITCHES

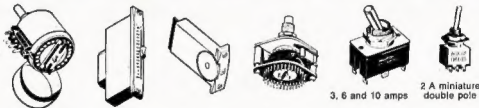

3, 6 and 10 amps

2 A miniature double pole

Other Painton components include: RF Chokes, Knobs, Dials, Pointers, Spring Loaded Terminals, "Camblock" Terminal Strips, Relays.

**PAINTON are distributors in Australia for the following high grade components:**

### ALCOSWITCH

Sub-miniature switches and knobs.

### PARKER

The 10,000% overload meter.

### DIGITIZER

Decade and binary thumb-wheel switches.

### DAVALL

Moulded track, carbon potentiometers.

## PAINTON (AUSTRALIA) PTY. LTD.

29 RAILWAY AVENUE, HUNTINGDALE, VICTORIA 3168. 'PHONE 569 0931

*Consult your PAINTON sales office for more detailed information.*



N.S.W. 2065  
6 Pacific Highway  
St. Leonards

43 2652

QLD. 4122  
7 Gralunga Street  
Mount Gravatt

49 5385

S.A. 5112  
11 Black Top Road  
Hillbank  
(Via Elizabeth Vale)  
55 6339

W.A. 6007  
Everett Agency Pty. Ltd.  
17 Northwood Street  
West Leederville  
8 4137

PA100

# VK3 V.H.F. GROUP TWO METRE CONVERTER

BY THE PROJECTS COMMITTEE OF THE VK3 V.H.F. GROUP

SINCE the development of a successful 6 metre converter by the then Converter Committee of the VK3 V.H.F. Group, a 2 metre converter has been developed. Design of a 432 Mc. converter is continuing. The design objectives for the 2 metre converter were:

- Best noise figure possible consistent with reasonable cost.
- Sufficient gain to allow use with tunable i.f. receivers of relatively low sensitivity, such as car radio receivers.
- Good cross-modulation characteristics.
- Adaptable to a wide range of i.f. output frequencies.

## DESIGN CONSIDERATIONS

Semiconductor devices that will outperform the best vacuum tubes are readily available at very attractive prices. Semiconductors are, therefore, the logical choice. There is little to choose between bipolar transistors and field effect transistors on the basis of noise figure. Noise figure is generally regarded as being the most useful figure of merit for devices to be used for v.h.f.-u.h.f. amplifier applications.

A brief discussion of noise may be in order. Any generated signal has associated with it an amount of noise. This noise is unavoidable, since it is generated by thermal agitation in the source impedance of the generator, for example the radiation resistance of an antenna. The theoretical limit to reception is the ratio of signal power to noise power, i.e. the signal to noise ratio.

Just what constitutes a minimum usable signal to noise ratio cannot be specified, since this depends on the type of signal and to a very large extent the person receiving the signal.

Noise figure is the amount by which signal to noise ratio is degraded after passing through an amplifier, and is given by the formula:

$$NF = 10 \log_{10} \frac{S_{pN_1}}{S_{pN_2}}$$

Where  $S_{pN_1}$  is the input signal to noise ratio.

$S_{pN_2}$  is the output signal to noise ratio.

In general, while the lowest possible noise figure is desirable at 144 Mc., there is a limit to the minimum useful noise figure. In addition to noise due to thermal agitation in the radiation resistance of the antenna and the input stages of the receiver, external noise is also received by the antenna. At 144 Mc. external noise is made up of man-made electrical noise, atmospheric noise and cosmic noise. In quiet locations cosmic noise is the limiting factor.

As the noise figure is lowered, noise introduced by the receiver becomes insignificant in relation to external noise, and further reducing the noise figure brings no real benefit.

In the practical case, lower noise figures may be necessary to overcome unusually high feeder losses.

The noise figure below which cosmic noise is the limiting factor is considered to be 2-2.5 db. at 144 Mc.

Accurate measurement of noise figure is quite difficult and the many pitfalls can give rise to conflicting or exagger-

Converter gain must be sufficient to override noise generated by the tunable i.f. and in addition must provide sufficient signal so that the total amplification makes any signal above the noise audible. Approximately 20 db. gain is quite adequate for use with any communication receiver, however since car radios and other less elaborate re-




ated claims about receiver performance. Noise figure is generally measured indirectly, by determining the amount of extra noise necessary to double the noise output of the receiver. The technique used must not rely upon assumed linearity of the receiver.

Equipment used to obtain noise figures quoted for prototypes was:

- Hewlett Packard noise source, diode type, HP343A.
- Hewlett Packard noise figure meter type HP340B (22 Mc. i.f.).

ceivers are likely to be used, considerably more gain than 20 db. is desirable. One microvolt into a converter with 35 db. conversion gain will produce an output of 87 microvolts at the i.f. frequency.

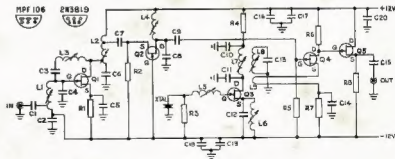Susceptibility to cross-modulation is determined by the shape of the transfer characteristic of the device concerned. Because of the approximate square law characteristics of FETs, their use significantly reduces cross-modulation problems.



Circuit of VK3 V.H.F. Group 2 Metre Converter

- |                     |              |                |                      |
|---------------------|--------------|----------------|----------------------|
| R1-220 ohms.        | C1-470 pF.   | C19-3.3 pF.    | G1-MPP106.           |
| R2-2.2K ohms.       | C2-100K pF.  | C20-1000 pF.   | C2-MPP106.           |
| R3-330 ohms.        | C3-470 pF.   | C13-3.3 pF.    | C3-2N3819.           |
| R4-470 ohms.        | C4-3.3 pF.   | C14-1000 pF.   | C4-MPP105.           |
| R5-100K ohms.       | C5-1000 pF.  | C15-4700 pF.*  | C5-2N3819.           |
| R6-10K ohms.        | C6-3.3 pF.   | C16-1000 pF.   | X21-See text.        |
| R7-10K ohms.        | C7-470 pF.   | C17-0.047 uF.* | Coil Data-See Table. |
| R8-3.9K ohms.       | C8-3.3 pF.   | C18-0.047 uF.* | Capacitors marked *  |
| Resistors 1/4 watt. | C9-470 pF.   | C19-1000 pF.   | Rad Cap., others     |
|                     | C10-1000 pF. |                | Disc. Ceramic.       |



For optimum performance, the lowest intermediate frequency is limited by the bandwidth of the converter. Noise is additive on a power basis and if the first image band falls within the bandwidth of the converter, image noise will add to noise already associated with the signal, reducing the signal to noise ratio. For the worst possible case signal to noise ratio may be degraded by 3 db.

## DESCRIPTION

In view of the above considerations, it was decided to use field effect transistors in the design. Evaluation of the specifications of available FETs resulted in the use of the MPF106 N-channel junction FET (Motorola) for r.f. amplifier and mixer functions. The 2N3819 N-channel JFET (Texas Instruments) was chosen for oscillator and source follower.

The first amplifier stage uses an MPF106/2N5485 (Q1) in neutralised common source configuration. Neutralisation could have been avoided by the use of dual gate metal oxide insulated gate FETs (MOS-FETs), however consideration of noise figure and the ease of neutralisation with the circuit used led to the choice of the MPF106 JFET. Neutralisation is accomplished by adjustment of L3, which resonates with the drain to gate feedback capacitance to form a high impedance parallel resonant circuit at 144 Mc.

Signal is taken from L2 in the drain circuit of Q1 via C7 to the source of Q2, a second MPF106. The second stage is in grounded gate configuration, forming with Q1 a shunt fed cascode r.f. stage. Signal is taken from L4 in the drain of Q2 via C9 to the gate of

Q4, the mixer. Oscillator injection is via a link on L8 into the source of Q4. Intermediate frequency output appears across R6 in the drain circuit of the mixer, while a direct coupled source follower (Q5) transforms the i.f. band to a low impedance for use with coaxial cable.

The crystal oscillator circuit requires some comment. A single FET is used as both oscillator and multiplier. The circuit is designed for use with third overtone crystals in the range 39-48 Mc. Adjustment of oscillator to exact frequency is possible with adjustment of L5. If this facility is not required, L5 may be replaced by a link and the value of R3 increased to 56K ohms.

The third harmonic of the crystal frequency is selected by L7. The double tuned circuit coupling of L7, L8, L9, results in a "clean" injection waveform at the source of the mixer. Fifth overtone crystals of about 61 Mc. have been used, with doubling in Q3, but insufficient information is available for success with this range to be guaranteed. No changes to coil dimensions were required.

A supply of 9-15v. at 10-20 mA. d.c. is required. The design voltage is 12v. Positive and negative supply rails are a.c. isolated from earth, giving greater flexibility in application. Should this not be required, the appropriate bypass capacitors may be replaced by short wire straps.

The converter is constructed on an epoxy fibre-glass printed circuit board 4" x 2½", which is the same size as the VK3 V.H.F. Group 6 metre converter. All capacitors below 100 pF. are NPO disc ceramics. Above 100 pF. Hi-K disc ceramics are used. Resistors used must

be of small physical dimensions. Ratings up to ¼ watt are suitable. The coil formers used are Neosid type A (single assembly) and the type B (double assembly) with screening cans. The bases usually provided have not been used, so as to maintain high unloaded tuned circuit Q. Instead, the boards are drilled 7/32" and the formers glued in. F29 v.h.f. slugs are used throughout. Coil dimensions are given

## PERFORMANCE

All prototypes were measured with noise figures in the vicinity of 2 db. The minimum noise figures of two of the prototype converters were 1.6 db.

The gain of the converter is adequate for all reasonable applications, with prototypes having measured conversion gains in excess of 35 db. With all tuned circuits peaked for 144.25 Mc., 3 db. bandwidth was 540 Kc. The noise figure was substantially constant over this range. The 10 db. bandwidth was 1.4 Mc. The bandwidth is quite adequate for operation in the normally used part of the band, and allows the use of i.f.s down to the broadcast band. Greater bandwidths may be obtained by stagger tuning, with some sacrifice in gain and noise figure.

No measurements of cross-modulation have been performed. Qualitative tests indicate that cross-modulation performance is very good. No diode protection at the input of the converter was found necessary, even when used with transmitters of over 100w. input.

## CONSTRUCTION

Complete construction details will be supplied with the kits which will be made available. For those not wishing to obtain the kit, a few hints may be helpful.


First, all minor components should be soldered in. Locating lands on the Neosid formers should be filed off and the formers glued in place with Araldite, making sure that the former lines up correctly with the position of the can.

Care must be taken when soldering in the FETs, to prevent damage due to excessive leakage current from soldering iron tip to earth if a Scope soldering iron is used. The board should be isolated from earth while soldering the FETs in place. No special precautions are necessary when handling the FETs used, however for best performance they should be pushed down to within 1/8" of the board. The FETs are guaranteed by the manufacturer to sustain 250°C. lead temperature 1/16" from the body for 10 seconds. A Scope soldering iron with clean, pointed instrument tip is suitable.

## ALIGNMENT

With supply connected to the completed converter, L5 and L6 should be tuned for maximum voltage across R4. The 5 volt range of a multimeter is suitable. Approximately ½ volt change should be evident. With the voltmeter connected across R7, L7 and L8 should be adjusted for maximum reading (approximately ½ volt change). Some particularly inactive crystals may be made to work by increasing the value of R3 from 390 ohms to 1K ohms.

## COIL DATA

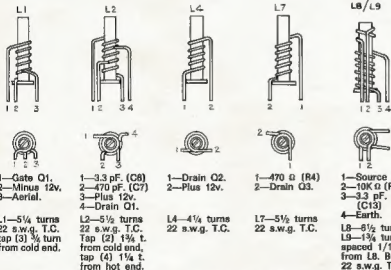

Connect antenna to converter and output of converter to the tunable I.F. Using a suitable signal source—signal generator, early stages of own transmitter or a strong local signal—adjust the other coils in order L4, L2, L1. If the converter oscillates adjust L3 to restore stability. Re-peak all coils and neutralising for best results. Final alignment may be carried out with a simple noise generator if available.

A number of kit sets have been made available to members of the VK3 V.H.F. Group. A further limited number of kits will be made available by post at a price of \$12.50 including postage. The kit is complete except for the crystal.

Because of the large number of specialised components, it was decided to make available the full kit comprising drilled board, resistors, capacitors, FETs, co-axial and crystal sockets, coil former assemblies and incidental bits.

Inquiries should be addressed to:

"Two Metre Converter,"  
W.I.A., Vic. Div.,  
P.O. Box 36, East Melbourne,  
Vic., 3002.

## OBITUARY

### MAX FOLLE, VK3GZ

The death occurred on 28th December of Max Folle, VK3GZ, at the age of 59. Born in Richmond, Victoria, in 1909, he was educated at Surrey Hills State School, Scotch College and the Royal Melbourne Technical School. He studied Radio Engineering and was an associate member of the Institute of Radio and Electronic Engineers of Australia. He joined the Wireless Institute of Australia in February 1948.

Max had many interests and although he had only limited time to devote to Amateur Radio, was at the time of his death trying to organise a radio club in MILDURA.

Max entered the field of commercial radio in 1932 when he was appointed engineer to 3YB, when he installed a station in a railway carriage which visited and transmitted from many country towns. He built the first equipment for 3MA Mildura when the station was formed in 1932. At the time of his death he was managing director of Sunraysia Television Ltd. STVB, with which company he had been for the last four years.

Members of the Wireless Institute of Australia regret the passing of another of our pioneers and extend their sympathy to his family.

## VK3 VHF GROUP

### 2 METRE CONVERTER

KITS AVAILABLE FOR THIS  
CONVERTER, \$12.50 each, post paid.

Cash with Order to:  
Victorian Division, W.I.A.,  
P.O. Box 36, East Melb., Vic., 3002.

May be some slight delays depending on arrival of components from overseas.


## FAIRCHILD WINS TOP AWARD

An advanced integrated circuit array developed by Fairchild Semiconductor was acclaimed as one of the 100 most significant technical products of 1968 in the Annual National Research Week competition held recently in New York.

Fairchild's winning entry was the 4500 Bipolar "Micromatrix" Array, a monolithic semiconductor device that provides the electrical equivalent of 352 transistors, resistors, diodes and other components, all interconnected to provide a desired function. "Micromatrix" is a new design technique that utilises computer aided design facilities to achieve low production costs and fast deliveries on order.

The 4500 "Micromatrix" Array is a highly complex unit, which incorporates a standard semiconductor base with unique two-level wiring interconnections, designed to a customer's specifications. It consists of eight distinct cells on a silicon chip, and, apart from its package, is no larger than the head of an ordinary pin.

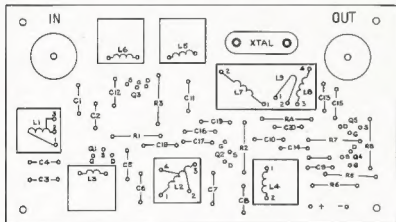The only integrated circuit among the 100 products selected, the 4500 features exceptional reliability and a high degree of logic compatibility with other circuits.



Layout of the VK3 V.H.F. Group 2 Metre Converter



Modified Printed Circuit Board of the VK3 V.H.F. Group 2 Metre Converter



## VK3 VHF GROUP

### 6 METRE CONVERTER

Transistorised Basic Kit, as detailed  
in "A.R." November, 1967.

FETs, Transistors, Coil Formers and  
Printed Circuit Board. No capacitors,  
resistors or crystal:

Basic Kit .... \$6.50, post paid  
P.C. Board .. ... \$1.50, post paid  
2 FETs for modified output, \$2 extra

# SOLID STATE COUPLING METHODS\*

The whys and wherefore of coupling circuits in solid state i.f. amplifier design

JOSEPH TARTAS, W2YKT

**A**BOUT seven years ago, I made a prediction in some material I was writing about t.v. servicing, that, "Undoubtedly transistors will eventually replace tubes in all of the t.v. circuits but the c.r.t. itself." Not only has this prediction come true, but at some future date, this may well be remembered, not as the Space Age, but as the Semiconductor Age. Each new development in the transistor line presents a different problem to the circuit designer; the bipolar transistor, the FET and the IC.

As the usable frequency spirals upwards, the input and output circuits must be altered to compensate for different input and output impedances. Input, output and feedback capacitances (by whatever the name) and methods of coupling to achieve the desired gain and bandpass characteristics also change.

## COMPARISON TO VACUUM TUBE I.F. CIRCUITS

The transistor has been considered as essentially a current amplifier. As an i.f. amplifier, however, its sole purpose is to provide a sufficiently high voltage level at the detector input. It may be regarded, except for the considerations to follow, to be similar to vacuum tube voltage amplifier circuits.

Tubes have relatively high input and output impedances. Bipolar transistors, in the more useful configurations, have high output impedances (although considerably lower than that of tubes), but, unfortunately, have quite low input impedances. FETs on the other hand, have semiconductor characteristics, but with impedances higher even than vacuum tubes.

Because the transistor is basically a power amplifier, the maximum transfer of power occurs when the coupling network is matched, both to the output of one stage and input of the next stage. In addition to impedance matching, the resonant frequency of any tuned circuit connected to the transistor must be considered. The output capacity of most transistors is low, but the input capacity is often higher than those of tubes, as much as 30 pF. In some types. These capacities must be considered since they are part of the total tuning capacity across the coils in i.f. amplifiers.

Of the three possible circuit configurations, common-base, common-emitter, and common-collector, the common-emitter circuit is almost exclusively used for i.f. circuitry. It is the common emitter circuit that produces a high voltage gain as well as the greatest power gain of the three configurations.

Another advantage in using the common emitter circuit is the possibility of isolation due to the physical layout

of the transistor terminals. Reference to Fig. 1 shows that a shield partition may be used to completely isolate the input circuit consisting of the base circuit (which is also the collector or output circuit if another stage precedes it) and the emitter circuit, from the output, or collector circuit. In tetrode transistors the additional lead does not prevent use of the shield, but also provides a separate element for a.g.c. control that is completely isolated from the active r.f. circuit elements.

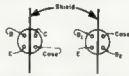


Fig. 1—Schematic diagrams of most transistors are alike except for the ground lead or the extra base connection in the tetrode.

Until recently, the collector of a triode transistor was tied to the case and presented a problem in shielding. Now, many r.f./i.f. types have the case isolated from the transistor elements and it can be grounded through a fourth lead connected to the case.

## OUTPUT CIRCUITS

The output impedance of the transistor in an L-C tuned amplifier is sufficiently high that the tuned circuit could be represented as in Fig. 2, and is essentially the same configuration as for a vacuum-tube circuit. The value of R would be higher than the impedance of the L-C circuit or omitted, depending upon the desired loading, the loading effect of the collector, and the means by which it is coupled to the following base.

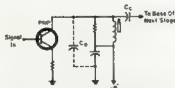


Fig. 2—Output circuit of a transistor i.f. stage. The output capacity is identified as  $C_c$ .

## INPUT CIRCUITS

In order that the low impedance input of the transistor does not excessively load the tuned circuits, thereby reducing the gain, some means of impedance matching must be resorted to.

There are three ways in which the proper match may be achieved. To better understand these methods, consider the various relations of the parallel tuned resonant circuit shown in Fig. 3.

$$\begin{aligned} \text{At Resonance: } & X_L = 2\pi FL = X_C = \frac{1}{2\pi FC} \\ \text{Unloaded } Q &= X_L/R = X_C/R \\ Z_{\text{resonance}} &= X_L C / I_0 = X_C L / I_0 \\ Z_{\text{resonance}} &= Q X_L = Q X_C \end{aligned}$$

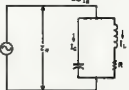


Fig. 3—A parallel tuned circuit and its various current, voltage and impedance relationships.

At resonance, the inductive and capacitive reactances are equal and the resonant impedance,  $Z_R$ , is the product of the coil Q (determining the bandwidth) and the reactance of either element since they are equal at resonance. The Q is the ratio of the tank current ( $I_L$  or  $I_C$ ) to the total current  $I$  divides, the ratio of the currents in each branch depends upon the ratios of reactance and resistance present in the tank circuit. If the generator is considered to have a very high impedance, then the signal may be injected between the common terminal and terminal 1, 2, or 3 in Fig. 4, without affecting the resonant frequency, unloaded Q, or resonant impedance of the tuned circuit, since  $Z_R = Z_L Z_C / Z_L + Z_C$  as in parallel resonance.

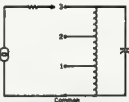


Fig. 4—Impedance matching by means of a tapped inductor. The tap impedance equals  $Z_t = (N_t/N)^2 Z_L$  where  $N_t$  is the number of turns from common and N is the total turns.

Since the inductance of a coil varies as the square of the number of turns, the inductance, and hence the reactance and impedance at points 1, 2, and 3, will be one ninth, four ninths, and the total impedance respectively. Other arrangements are equally possible, i.e. a centre tap gives one-fourth the total impedance, etc.

The tuning capacity (where used) may be employed in a similar way to divide the total impedance, as shown in Fig. 5A. If the resultant capacity is the tuning capacity, the r.f. voltage across the tuned circuit is divided in the ratio of capacitive reactance, or the inverse of the capacity ratios, since:


\* Reprinted from "CQ," July 1968.

$$\frac{IX_{C1}}{IX_{C2}} = \frac{E_1}{E_2}$$

$$\frac{X_{C1}}{X_{C2}} = \frac{1}{\frac{2\pi f C_1}{1}} = \frac{C_2}{C_1}$$

Stagger tuned i.f.'s, as found in t.v. circuits, use the tube capacity (plus strays) as the only resonating capacity. In transistor circuits the input capacity is often much higher, but as seen in Fig. 5B, this capacity may be used as part of the impedance divider. If this capacity is too small, additional cap-

$$E = E_1 + E_2$$

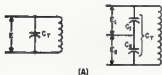

(A)

Fig. 5A.—Impedance matching by means of a capacitive divider.

acity may be used across the input, or the coupling capacitor that forms the other part of the divider may be made sufficiently small to give the proper division. When the tuning capacity consists mostly of a large fixed capacitor across the coil, this divider has little effect on the tuning if a small coupling value is used. See Fig. 6 for typical values.

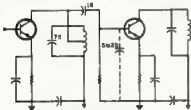


Fig. 5B.—Typical capacitor divider circuit and values.

## DOUBLE-TUNED CIRCUITS

Basically, the tuning and coupling of tuned pairs are accomplished the same way as for tube circuits. The only difference in their application to transistor circuitry is in the means of loading.

Fig. 7 shows the way in which a transistor with output impedance  $R_o$  and capacitance  $C_o$  is connected by means of a tap to the primary. The secondary is connected to another transistor stage with equivalent parallel input resistance  $R_i$  and capacitance  $C_i$ . The primary tap is usually at or near the top, due to the fairly high value of  $R_o$ . The secondary tap will normally be placed well below the middle of the coil to provide the desired amount of loading, since  $R_i$  is low, compared to  $R_o$ . The coupling may consist of either capacity or mutual inductance.

## SINGLE-TUNED TRANSFORMER COUPLING

An alternate method of matching a single tuned circuit to the input impedance of another transistor is by means of transformer coupling where the secondary and primary are tightly coupled but has a step down ratio. The step down ratio of the transformer should be equal to the square root of the ratio of output to input impedance of the transistors. This, in turn, gives the number of turns for the secondary, if the number of primary turns is already known. In this case the secondary is untuned, as shown in Fig. 8.

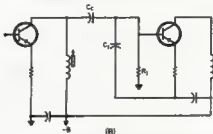


Fig. 5B.—Typical circuit uses the coupling capacitor.  $C_1$  and the input capacity  $C_i$  to form the impedance divider.

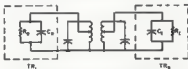


Fig. 7.—Equivalent circuit of input and output matching with a tuned pair. The coupling between the two coils is discussed in the text.

## NEUTRALISATION OR UNILATERALISATION

Unlike the vacuum tube, the transistor is not a unilateral device, i.e. current can flow in both directions, even though small. Because it can do this, the output voltage variations cause variations at the input of the same transistor. The result is a feedback voltage that is, unfortunately, in phase and therefore regenerative. If this feedback voltage is large enough, the amplifier goes into oscillation. Just as in tube amplifiers, the feedback is large at higher frequencies, and if the frequency is low enough, the feedback voltage is too small to be of consequence. The equivalent feedback circuit of the common emitter circuit of Fig. 9A is shown in Fig. 9B.

The capacity of the base-collector junction,  $C_{bc}$ , is small and of little consequence at low frequencies. The resistor it shunts,  $R_{bc}$ , is very high and is of little consequence under normal operation when reverse bias is applied to the base-collector junction. As the




Fig. 8.—Transformers with untuned secondaries are often used for impedance matching. The formula governing the relationship between the primary and secondary impedances is shown above.

frequency increases, the capacitive reactance decreases, until such a frequency is reached where the impedance becomes lower than the value of  $R_{bc}$  and feedback occurs. The base spreading resistance  $R_{be}$  produces a positive feedback voltage due to the collector current passing through  $C_{bc}$ .

Since we are interested in the use of these circuits at reasonably high frequencies some means must be used to prevent the occurrence of regeneration and oscillation. This method is known as **unilateralisation** when all the input changes due to feedback, both resistive and reactive are cancelled. If only the reactive changes are cancelled, they are said to be **neutralised**.



(A)

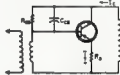

(B)

Fig. 9A.—Simplified common emitter amplifier. Fig. 9B.—Common emitter equivalent high frequency circuit showing the elements that produce feedback.

To some readers who are familiar with transmitter circuitry, the methods used for unilateralisation and neutralisation will be familiar. For reasons previously given, the common-emitter amplifier only will be discussed, although the following methods will apply equally to the common-base amplifier.

Fig. 10 shows a typical i.f. stage using transformers with untuned secondaries for the input and output circuits. The input signal is a.c. coupled by means of the step down secondary winding, through the d.c. blocking capacitor,  $C_b$ , to the base. The transistor is forward biased by means of the resistor  $R_b$  and the supply voltage. This provides the proper bias voltage between the base and emitter. The

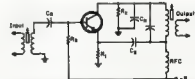


Fig. 10.—Typical i.f. amplifier stage unilateralized by partial emitter degeneration. Components  $R_1$ ,  $R_2$  and  $C_1$  form the unilateralizing network.

unbypassed resistor,  $R_1$ , in the emitter provides degeneration and reduces the positive feedback produced in the base spreading resistance within the transistor structure itself. Resistor  $R_2$ , in conjunction with  $C_{bc}$ , the neutralising capacitor, produces an additional negative feedback due to collector current that is directed back to the emitter.

(Continued on Page 35)

# PUTTING THE GELOSO G222 ON 160 METRES

J. A. ADCOCK,\* VK3ACA

IN view of the general acceptance of the sideband and the prospect of the Geloso becoming obsolete, it was decided to carry out modifications to make it more versatile. Rather than shelve or sell a useful piece of equipment, it can be adapted to perform a function not normally covered by the s.s.b. transceiver. Although modifications were carried out to a complete Geloso transmitter, the information should be of equal interest to people with the Geloso v.f.o. only. The observations on stability should be of interest together with others recently appearing in this magazine.

The aim of the modifications were:

1. Introduce coverage of the 160 metre band without altering the existing coverage of six bands or the v.f.o. calibration.
2. Improve the general stability of the v.f.o.

It might be considered unnecessary to preserve operation on the 27 Mc. band, however it was found practical to retain this band without introducing an extra switch position. Under the re-arranged scheme both band switches, exciter and final, have been altered as follows:

Band	Old Scheme	New Scheme
1	80 mx	160 mx
2	40 mx	80 mx
3	20 mx	40 mx
4	15 mx	20 mx
5	11 mx	15 mx
6	10 mx	11 & 10 mx

## MODIFICATIONS TO THE FINAL TUNING

It is quite simple to cover 10 and 11 metres on the one tap of the final tuning tank. The 11 metre tap was removed completely. In this case it was found desirable to re-locate the 10 and 15 metre taps at points indicated in Fig. 1.

An extra coil must be wound for the 160 metre band. With the existing tuning capacitor, the L/C ratio was found to be too high and thus an extra capacitance must be switched in parallel with the

allev. To achieve this, an extra switch wafer was added to the final range change switch. This is fairly easy to do if one has an old two-bank 6 or 12 position Oak switch. I was fortunate in having such a switch with a ceramic wafer which was ideal for the purpose.

Having the spare switch and using some of the parts of the existing switch, including the tap shorting wafer, it is not difficult to engineer the new switch (Fig. 3). It will probably be necessary to use the new clicker plate and shaft because of the unusual driving shaft on the original switch. To engage the original wafer a double flat should be filed on the switch end of the shaft.

The extra coil was wound on a 14" diam. bakelite tube (Fig. 2) and this was mounted vertically between the 6146, the tuning capacitor and the filter capacitor. It was attached to the chassis by means of a right angle brass bracket. The actual winding was close to the top end of the former and mounted so that it was close to the end of the existing coil.

Having made coil, obtained the extra capacitors and re-modelled the switch, one should proceed as follows (see Fig. 1).

Remove all taps from the switch except the 10 metre tap. Discard the 11 metre tap and shift all remaining taps around one position on the switch. Connect the lower end of the new coil to the 80 metre end of the old coil and the free end of the new coil to the shorting wiper of the switch. Connect the ceramic capacitors so that they are switched in parallel with the tuning capacitor in the 160 metre position.

It should also be noted that the variable coupling capacitor may have to be considerably greater on 160 metres. In this case the extra capacitance was included in the aerial tuning unit.

## ALTERATIONS TO EXCITER

At first sight it might appear necessary to provide a completely new oscillator section, however if the 3.5 to 4 Mc. coil is removed and replaced by one

tuned circuit as either a straight amplifier or doubling to 3.5. (The terminology used here is that used in the Geloso manual.) The same scale can still be used for 3.5 to 4 Mc. and an extra scale can be marked below this scale from 1.8 to 1.9 Mc., exactly half 3.8 to 3.9 Mc.

In the new arrangement two extra coils must be introduced; one to cover 1.8 Mc. at the driver stage and an extra tuned circuit for 3.5 Mc. at the intermediate tuning position. At this position resistance coupling was tried, but this was inadequate at 3.5 Mc. In the original circuit, this stage is tuned by internal capacitance of the coil only. It was found to be impossible to make the new coil for 3.5 Mc. resonate in this way, but the non resonant coil was found to be quite adequate

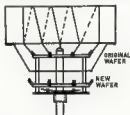


FIG. 3 EXISTING TANK COIL

The new oscillator coil for 1.75 Mc. was wound on a fairly large diameter former, and after some experiment, with a slug. In this case it was found to be best in the interests of stability. The absence of a slug does introduce some difficulty in tuning and to this end one turn may have to be either added or removed to obtain the correct scale law in conjunction with the trimmer. Having settled on the new coil, the trimmer should be satisfactory for frequency adjustment.

Table 1 is a tabulation of original and new circuit tuning ranges.

Band	Intermediate		
	Oscillator Mx	Self Reson. Mc.	Driver Mc.
Old arrangement:			
80	3.5-4.0	resistance	3.5-4.0
40	3.5-3.85	7.0-7.3	7.0-7.3
20	" "	" "	14.0-14.8
15	" "	" "	21.0-21.9
11	6.74	13.48-13.6	26.96-27.23
10	7.425	14.0-14.85	28.0-29.7
New arrangement:			
160	1.75-2.0	resistance	1.75-2.0
80	" "	3.5-4.0	3.5-4.0
40	3.5-3.85	7.0-7.3	7.0-7.3
20	" "	" "	14.0-14.8
15	" "	" "	21.0-21.9
11, 10	6.74-7.425	13.48-14.85	26.96-29.7

Table 1.

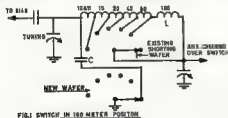


FIG. 1 SWITCH IN 160 METER POSITION

C—New capacitor, 200 pF. low K high voltage ceramic.

Tapping points:

10 and 15 metres—turn 4.

15 metres—turn 6.

20 to 80 metres—no change.

L—New coil, 25 turns of 22 B & S., close wound, on a 1 1/2 inch bakelite former.



FIG. 2 EXTRA TANK COIL

of four times the inductance, without changing any capacitance values, exactly half the frequency and range will be covered, namely 1.75 to 2 Mc. It is now possible to cover the 80 and 160 metre bands with the same oscillator coverage, using the "intermediate"

\*P.O. Box 106, Preston, Vic., 3072.



## EXCITER MODIFICATION PROCEDURE

Wind the coils as described in Fig. 4. First let us deal with the driver tuning and switch wafer No. 3. Remove the 11 metre connection to the switch and shift all connections around one step, leaving the first position vacant. It will be noticed that the shorting sector does not bridge position No. 5 (now 15 metres), but this is of little consequence. Place the new coil L12 in a position between L10, the frame and wafer No. 3. The coil will be found to work satisfactorily although there is only  $\frac{1}{8}$ " space. (Note position 1 is taken as the 160 metre end of the switch.)

Next let us deal with the intermediate tuning position and switch wafer No. 2. This 11 metre tap on L4 must be disconnected. Some attention must be paid to the shorting sector on the back of the switch. Although not shown in the circuit diagram, this section is used to short out L5 when not in use. In the new circuit this would short out L5 in the 15 metre position. It is easily disconnected by bending the contact clip back out of the road on the shorting side of the switch. This is most important. (It is the only contact clip in use on this side.)

Shift connections from L5 around one step, the circuitry remaining unaltered, and leave the resistor in position 1 intact. This leaves the second position vacant.

The 3.5 Mc. oscillator coil occupies the position in front of the coil line up and this should be removed in order

to wind L11. Shift coils L1 and L3 along one position, leaving a gap between L3 and L4. Into this gap is placed the new L11 which has been wound on L2 former. L1 and L3 may both be replaced as discussed in the section on stability. L11 is wired into the circuit with its associate resistor to the vacant position 2 on bank 2.

## OSCILLATOR CONVERSION

Lastly, let us deal with the oscillator conversion and switch wafer No. 1. It is necessary to locate the new oscillator coil as far from the sides of the shield box as possible and as close to all associate circuitry as possible. The earth point of the 1,000 pF. mica capacitor must be moved to the tag strip directly across N555 to make extra space.

In this case the new L2A coil is placed directly in front of the cord drive spindle and close to L3 and the 6CL6 socket. There is still room for two new coils, L1A and L3A if required. L1A next to L2A and between the 1,000 pF. mica capacitor and the cord drive shaft, and L3A somewhere in between the old position of L1 and L2.

Connections to No. 1 wafer of the switch: The 11 metre connection is removed and connections to L1 are moved around one position, the new L2A is connected to positions 1 and 2 of switch wafer.

## STABILITY

There has always been some problem of stability in this unit and the following points were noted. The new coil L2A was much more stable than the old L1 coil, especially when using no slug. This latter effect could have been a characteristic of the coil former and slug type used. However, the larger the diameter of the coil the more stable the results. It was decided to try a new coil L1A and a similar improvement was observed.

It was also observed that there was considerably more erratic drift with the shield box in place. This defect was found to be due to intermittent contact around the perimeter of the shield. This problem was overcome by lining all contact surfaces with cellulose tape so that it only made contact with the two attaching screws.

## TUNING

The intermediate and driver tuning is quite straight forward and can be carried out with slug adjustment. There was some lack of drive at the ends of the range 27 to 29.7 Mc. and if it is necessary to fully cover this range, a two-coil resonant circuit could be tried at the intermediate position. With L1A peaked on 28 Mc. there was sufficient drive between 27 Mc. and 29 Mc.

There are some problems in tuning the new oscillator coils without a slug. The tuning range on each band is dependent on a balance between the inductance of the coil and the capacitance of the variable trimmer. The

simplest way to correctly tune the coils is, before removing the old coil, correctly adjust the variables to give the correct scale calibration. Wind the new coil and remove turns until the frequency at the bottom end of the scale is the same as before. Final check must be made with the cover in place.

It is not possible to get the frequency exactly as before and any small error can be corrected for with the trimmer.

If it is found that the tuning range is either longer or shorter than the calibrated scale, further adjustments must be necessary. Starting with the low end frequency adjusted correctly with the trimmer, if the top end frequency falls short of the calibration mark, turns must be removed from the coil and the trimmer re-adjusted. Conversely, if the top end frequency falls past the calibration mark, turns must be added. This is a tedious job and must be carried out with patience. If adjustments as described in the previous paragraph are carried out, these extra adjustments should be unnecessary.

This article should be of interest to most people with Geloso's, so good luck with your conversions and see you on 160 metres.

## CHANGE OF ADDRESS

W.I.A. members are requested to promptly notify any change of address to their Divisional Secretary—not direct to "Amateur Radio."

## W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. Position in the list is determined by the first number shown. The first number represents the participant's total countries less any credits given for deleted countries. The second number shown represents the total D.X.C.C. credits given, including deleted countries. Where totals are the same, listings will be alphabetical by call sign.

Credits for new members and those whose totals have been amended are also shown.

### FIGURE

VK6MS	315/330	VK3AB	286/314
VK3AO	312/338	VK3CJ	284/350
VK8RU	308/333	VK4TY	275/278
VK4HR	304/323	VK3TL	271/277
VK3AK	304/323	VK3APK	268/274
VK3JZ	303/330	VK2AAK	265/275

### New Member:

Cert. No. 33 VK4XY 115/119  
Attendance:  
VK3EZ 197/300

### O.V.

VK3QL	300/322	VK3YL	286/293
VK3AHQ	288/306	VK3BX	256/275
VK4PZ	280/314	VK3R	254/288
VK3CK	229/313	VK3APK	253/273
VK3AGH	282/296	VK3NC	264/277
VK4HR	279/299	VK3KD	253/277

### New Member:

Cert. No. 84 VK3XJ 124/130

### OPEN


VK3AGH	311/321	VK4TY	301/315
VK8RU	310/335	VK4PZ	298/322
VK4HR	309/333	VK3ARX	289/289
VK3AK	305/334	VK3TL	287/293
VK3CJ	304/332	VK3APK	286/288
VK3EO	302/325	VK3CB	288/274

### New Member:

Cert. No. 115 VK3XJ 186/173
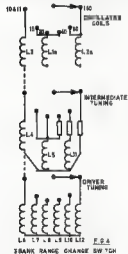
## AMATEUR FREQUENCIES:

ONLY THE STRONG GO ON—  
SO SHOULD A LOT MORE  
AMATEURS!



Refer to manual for details.

- COIL DATA** (Coils not listed remain unaltered):  
L2A replaces L2. Wound  $\frac{1}{4}$  in. from the top of  $\frac{1}{4}$  in. diam. polythene former; total height  $1\frac{1}{2}$  in., wind  $\frac{1}{4}$  in., close spaced, 34 B. & S. enamel wire. Remove turns as required.  
L1A (optional, see notes on stability) replaces L1. Wound  $\frac{1}{4}$  in. from the top of  $\frac{1}{4}$  in. diam. polythene former; total height  $1\frac{1}{2}$  in.; wind 26 turns of 28 B. & S. enamel wire. Remove turns as required.  
L11—Wound on former of old L2, retain slug tuning. Fill winding space with a single layer of close spaced 34 B. & S. enamel wire.  
L12—Wound on a 7/16 in. diam. slug tuned former. Wind  $\frac{1}{4}$  in. of a single layer of close spaced 34 B. & S. enamel wire.  
L4—Leave off 11 metre tap.



# PROJECT—SOLID STATE TRANSCEIVER

## PART FOUR

H. L. HEPBURN,\* VK3AFQ, and K. C. NISBET,† VK3AKK

This month's article will deal with five separate functions:

- The filter pre-amplifier.
- The transmitter mixer pre-amp.
- The carrier oscillator/BFO.
- The product detector.
- The balanced modulator.

Although these functions will be described separately, they are in fact combined on to three printed circuit boards. One board contains the filter pre-amplifier and the transmitter mixer pre-amplifier, a second p.c.b. houses the carrier oscillator/BFO and an amplifier while the third board contains the product detector and balanced modulator.

The second and third boards are housed in a 6½ x 4½ die cast box to prevent radiation into the rest of the circuitry of the transceiver.

### THE FILTER PRE-AMPLIFIER

The prime function of this module is to raise the output of the balanced modulator to a reasonable level prior

which, in series, tune the drain coil L23 to 9 Mc.

The function of D6 is explained later in this article, but D7 and D8 need comment.

When in the "receive" mode the amplifier gets its h.t. from the a.g.c. rail and its gain is thus controlled by the a.g.c. system. The a.g.c. rail, however, is only operative on receive. On transmit the amplifier is fed from the transmit h.t. line and is not a.g.c. controlled.

On receive diode D7 gates the a.g.c. "h.t." voltage to the amplifier while D8 prevents excitation of any transmit functions through the supply line.

On transmit, the situation is reversed with D8 conducting and D7 blocking off the a.g.c. rail.

### THE TRANSMITTER MIXER PRE-AMPLIFIER

This stage is used to raise the 9 Mc. s.s.b. output from the filter board to a suitable level for the various transmitting mixers.

Two courses of action were available. Either the low level s.s.b. output from the filter could be mixed to signal frequency and then amplified or it could be amplified first and then mixed to signal frequency.

The latter course was chosen on the grounds of economy for, since there is a separate mixer/pre-amplifier for each Amateur band, it would otherwise have been necessary to use four additional amplifier stages rather than one. It is also simpler to provide gain at 9 Mc. than at the higher Amateur frequencies.

As shown in Fig. 11 the amplifier consists of a Motorola 1550G integrated circuit and a 2N3564 emitter follower.

Input from the filter board is "gated" by D9 to a low impedance link on T4. The secondary of T4 is tuned to 9 Mc. by the 68 pF. parallel capacitor.

Output from the i.c. is capacitively coupled to the base of the 2N3564 emitter follower, the collector of which is earthed for r.f. by the 5 uF. tantalum capacitor.

Output is approximately 1.5 volts peak to peak into a 100 ohm load.

When H.T. is applied to the unit on transmit, diode D8 is switched on, allowing signal to get to the i.c. On receive, this h.t. is removed, D8 is switched off and the i.c. effectively isolated.

### THE CARRIER OSCILLATOR/BFO

Fig. 12 gives the circuit diagram from which it can be seen that each carrier crystal has its own circuitry, the outputs from the two oscillators being combined and fed to a simple resistance coupled amplifier. Each oscillator output is independently adjustable and, at maximum settings, is sufficient to give 6 volts peak to peak output from the amplifier. In this design only a portion of this output is used but is mentioned in view of the

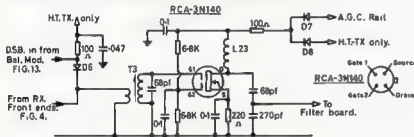


FIG. 10. 4 BAND TRANSISTORISED TRANSCEIVER - FILTER PRE-AMPLIFIER.

T3—Secondary is 40 turns of 33 gauge B. & S., close wound on Neosid 722/1 coil form and F29 slug.

L23—40 turns of 33 gauge B. & S., close wound on Neosid 722/1 coil form and F29 slug.

to the filter. However, the unit performs several quite important secondary duties in that it provides a suitable point at which to carry out TX/RX diode switching and, also, provides additional gain on receive.

While the amplifier is certainly necessary on transmit, it is possible that, when constructing only a receiver, it would not be required. However, since it was needed for the transmitter it has been used on receive as well.

The circuit is given in Fig. 10 and uses an R.C.A. dual gate 3N140 FET as a 9 Mc. amplifier. It does not require neutralisation.

Gate 2 of the 3N140 is held at half rail potential by the 6.8/6.8K divider, but is earthed for r.f. by the 0.1 uF. by-pass.

Output to the filter board at low impedance is taken from the junction of the 68 pF. and 270 pF. capacitors

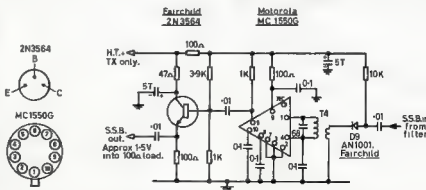


FIG. 11. 4 BAND TRANSISTORISED TRANSCEIVER - 9 MHz TX AMPLIFIER.

T4—Secondary is 40 turns of 33 gauge B. & S., close wound on Neosid 722/1 coil form and F29 slug. Primary is 10 turns of 33 gauge B. & S., close wound over cold end of secondary.

\* 4 Elizabeth Street, East Brighton, Vic. 3187.  
† 25 Thames Avenue, Springvale, Vic. 3171.

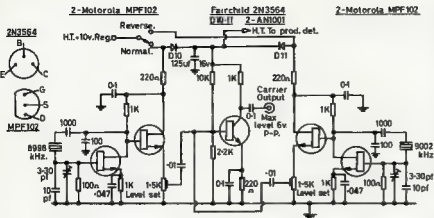


FIG. 12. 4-BAND TRANSISTORISED SIDEBAND TRANSCEIVER-CARRIER OSCILLATOR.

possibility of using the board as the basis of, say, a 7 Mc. crystal controlled transmitter.

The 3-30 pF. trimmers associated with each crystal allow some adjustment of the carrier frequency so that it may be correctly placed on the skirt of the filter. This adjustment, incidentally, is very simple. A signal is tuned in on the receiver and the trimmer adjusted for best speech quality.

Each oscillator consists of a MPF102 FET direct coupled to a second MPF102 used as a source follower. The source follower acts both as a buffer stage and as a means of presenting a suitably low output impedance to the 2N3564 amplifier. The crystal is used in its parallel mode with the feedback path being provided by the 100 pF. capacitor and the parallel combination of the 3-30 pF. trimmer and the fixed 10 pF. capacity.

In other applications, using crystals of different type and frequency, it may be necessary to adjust the fixed parallel capacity.

The amplifier calls for little comment except to point out the absence of any tuned circuits. The switching involved does, however, need explanation.

As stated earlier in this series of articles, the upper sideband crystal on 8998 Kc. is the one normally used on all bands, the correct sideband for the frequency in use being automatically selected by the correct choice of the heterodyning frequency in the injection chain. The "other" sideband for the band in use is selected by changing the carrier oscillator frequency.

H.T. is fed to either of the diodes D10 and D11 by the sideband selector switch. This switch thus chooses either the "normal" or "other" sideband for the frequency in use. If the "normal" sideband is selected then D10 will

conduct and energise the 8998 Kc. oscillator while D11 blocks off voltage from the 9002 Kc. oscillator. The position is reversed if the "other" sideband is selected.

The anodes of D10 and D11 are common and from this common point h.t. for the 2N3564 amplifier and the product detector is taken.

Direct switching of the two carrier crystals could have been used but this would have meant that the physical location of the carrier oscillator/BFO would have been fixed by the switch shaft and the flexibility of this design—and the ability to set the correct output levels would have been lost. As described, all switching is done in the h.t. line and, being "cold", the switch can be placed anywhere.

## THE PRODUCT DETECTOR

The circuit of the product detector is shown on the right hand side of Fig. 13.

A 9 Mc. signal from the carrier oscillator (Fig. 12) is applied to the junction of two 0.01  $\mu$ F. capacitors. The right hand path takes this signal to gate 2 of the 3N140 dual gate FET detector.

The 9 Mc. s.a.b. signal from the i.f. strip (Fig. 9, Jan. 1968 "A.R.") is applied to gate 1 of the device via an 0.01  $\mu$ F. capacitor.

Audio output is developed across the 2.2K drain load and unwanted products are filtered out by the 2.2K/1000 pF/2200 pF. combination.

H.t. filtering is provided by the 100 ohm resistor and 100  $\mu$ F. condenser. This h.t. is applied only on receive and only when receiving sideband or c.w.

## THE BALANCED MODULATOR

The circuit of the balanced modulator is shown on the left hand side of Fig. 13.

9 Mc. from the carrier oscillator/BFO is applied to a 2N3564 phase splitter to

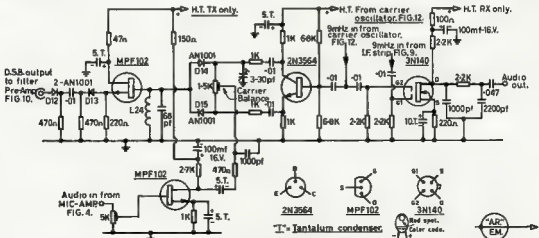


FIG. 13. PRODUCT DETECTOR & BALANCED MIXER-4 BAND TRANSISTORISED TRANSCEIVER.

L24—40 turns of 33 gauge B. & S. enamel, close wound on Neosid 722/1 former, F29 slug.

give two equal, but 180° out of phase, signals to the balanced modulator. The balanced modulator itself consists of two Fairchild AN1001 silicon diodes.

Audio from the microphone pre-amplifier board is applied via the 5K pre-set level control to a resistance coupled MPF102 amplifier, the output of which is filtered and applied to the slider of the 1500 ohm carrier balance control.

When audio is applied to the balanced modulator it becomes unbalanced for r.f. at an audio rate and the resultant, carrier free, double sideband signal passed via the MPF102 source follower to the filter pre-amplifier.

Diodes D6 (Fig. 10), D12 and D13 are used as isolating switches.

On transmit, h.t. is applied to D6 causing it to conduct and pass signal from the balanced modulator to the filter pre-amplifier. Because a d.c. path exists to D12, it also switches on and passes signal from the source follower to D6. As h.t. is applied to the source follower on transmit only, it is acting as a further gate. D13 prevents signal from the receiver from reaching the source follower on receive.

This long chain of diode gates is necessary to prevent any signal from the balanced modulator or carrier oscillator finding its way into the i.f. strip on receive. In view of the high gain of the whole i.f. chain it was not considered that the simpler (but probably more costly) approach of switching by relay would have been successful due to leakage across the relay contacts.

If the circuitry of the carrier oscillators, the product detector and the balanced modulator are viewed outside the context of the transceiver being described, it will be seen that they represent a fairly flexible series of "packages" which can be used on their own for incorporation in other end products.

It was mentioned above that one side of the carrier oscillator could be used,

with or without the amplifier, as a basis for a simple crystal controlled transmitter. Use of both sides of the board would extend this possibility to a dual frequency transmitter.

The product detector could be used on its own in other equipment and the balanced modulator could also be used in other circuits—with or without the source follower and/or switches and/or audio pre-amplifier.

#### AVAILABILITY

The above units are available in kit form, or as p.c.b.'s only, from 4 Elizabeth St., East Brighton, Vic., 3187. Prices are as follows:

- Filter pre-amp. and tx pre-amp., \$17.50 plus 13c postage.
- P.c.b. only, \$2.00 plus 5c postage.
- Carrier oscillator, balanced modulator and product detector complete in die cast box, \$28.50 plus 30c postage.
- Carrier oscillator and amp. p.c.b., \$2.00 plus 5c postage.
- Product det. and balanced mod. p.c.b., \$2.00 plus 5c postage.
- Any set of instructions, \$1.00 plus 5c postage.



### SOLID STATE COUPLING METHODS

(Continued from Page 10)

The blocking capacitor  $C_s$  in the emitter circuit keeps the supply voltage off of the emitter, and the r.f. choke keeps the emitter above a.c. ground. As a result, the positive feedback is just equal to the negative feedback, and the net result is zero, or unilateralisation.

#### BRIDGE NEUTRALISATION

The use of bridge neutralisation for transmitter amplifiers is well known,

and has been applied without difficulty to transistor amplifiers. The equivalent resistance and capacitance of the feedback circuits have already been shown in Fig. 9. If these elements are made part of a bridge circuit, and other circuit elements are used as the other arms of the bridge, the entire circuit becomes balanced (as far as the feedback voltages are concerned) and the result is unilateralisation. A typical amplifier using such a bridge circuit is shown in Fig. 11A. The components that make up the bridge circuit are shown in Fig. 11B.

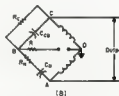
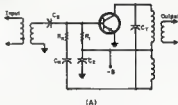


Fig. 11.—(A) Bridge unilateralisation and its equivalent circuit shown in (B).

When the ratio of the voltages in the arms A-B, B-C equal the ratio in arms C-D, D-A, no output voltage appears between B-D and the bridge is balanced. Because the phase shift is also balanced, the circuit is **unilateralised**. If a capacitor alone was found to be sufficient ( $C_s$  in the bridge arm) it would be **neutralised**.

## LOCALLY AVAILABLE V.H.F. FIELD EFFECT TRANSISTORS

Number	Type of FET	Package	Cost*	Noise Figure (db.)			Gain (db.)			Forward Transfer Admittance $Y_{fs}$ (mmhos) Freq. 1 Kc.	Reverse Transfer Capacitance (pF.) $C_{rss}$
				Freq.	Typical	Max.	Freq.	Min.	Typical		
2N3819	Junction	Plastic	\$1.60							2 to 6.5	4 pF. max.
MPF102	Junction	Plastic	\$1.15							2 to 7.5	3 pF. max.
2N4224	Junction	Metal	\$3.00	200 Mc.		5 db	200 Mc.	10 db.		2 to 7.5	2 pF. max.
TIS34	Junction	Plastic	\$2.00							3.5 to 6.5	2 pF. max.
2N3823	Junction	Metal	\$5.38	100 Mc.		2.5 db.	100 Mc.	18 db.	23 db.	3.5 to 6.5	2 pF. max.
MPF106/2N5485	Junction	Plastic	\$1.40	100 Mc.	1.6 db.	2 db.	100 Mc.	18 db.	23 db.	2.5 to 8	1.2 pF. max.
MPF107/2N5486	Junction	Plastic	\$1.50	400 Mc.	3.3 db.	4 db.	400 Mc.	10 db.	14 db.	4 to 8	1.2 pF. max.
TIS88/2N5245	Junction	Plastic	\$3.20	100 Mc.	1.6 db.	2 db.	100 Mc.	18 db.	23 db.	4.5 to 7.5	1 pF. max.
3N140	Dual Gate MOS FET	Metal	\$2.13	400 Mc.		4 db.	400 Mc.	10 db.		6 to 18	0.03 pF. max.
				200 Mc.	3.5 db.	5 db.	200 Mc.	15 db.	19 db.		

\* Single unit price including sales tax. (Prices believed to be correct at time of compiling table.)

This table was compiled from manufacturers' data by Eric Gray, VK2SSG.

## B.A.R.T.G. SPRING RTTY CONTEST

### 1959 RULES

When. 0200 G.M.T., Saturday, 15th March, until 0200 G.M.T., Monday, 17th March, 1959. The total contest period is 48 hours, but no more than 24 hours of operation is permitted. Times spent in listening counts as operating time. The 12 hour non-operating period can be taken at any time during the contest, but "off periods" may not be less than two hours at a time. Times on and off the air must be summarised on the Log and Score Sheets.

Hands. 2.5, 7, 14, 21 and 28 Mc. Amateur bands.

Stations may not be contacted more than once on any one band. Additional contacts may be made with the same station if a different band is used.

Country Status. A.R.R.L. Country List, except KL7, KH8 and VO to be considered as separate countries.

Messages exchanged will consist of: (a) Message number, (b) Time G.M.T., (c) Country and call sign.

### Points:

- All two-way r.t.t.y. contacts with stations within one's own country will earn TWO points.
- All two-way r.t.t.y. contacts with stations outside one's own country will earn TEN points.
- All stations will receive a bonus of 200 points per country including their own.

### Scoring:

- Two-way exchange points times total countries worked.
- Total country points times number of continents worked.
- Add (a) and (b) together to obtain your test score.

### Sample score:

- Exchange points (202) times countries (10) equals 2020.

(b) Country points (2000) times continents (3) equals 6000.

(c) (a) and (b) added to give a score of 8020 plus 6000 equals 14020.

Logs and Score Sheets. Use one log for each band and indicate any rest periods. Logs to contain band, message number, time, G.M.T. and continents. Exchange points claimed. All Logs must be received by 24th May, 1960, to qualify.

Awards: Certificates will be awarded to the two top scorers in each country. The judges' decision will be final and no correspondence can be entered into in respect of incorrect entries. This is to enable the scores to be worked out more quickly and should result in more speedy publication of the results.

Send your Logs to, Ted Double, GACDW, B.A.R.T.G. Contest Manager, 338, Windmill Hill, Enfield, Middlesex, England.

### 1959 RESULTS

The results of this contest have been received, but in view of the limited Australian participation, we will not publish the list.

Suffice to say, VK3KF finished 25th in the single operator section with a score of 25,000 points, and VK3DM was 1st in the multiple operator section with a score of 33,794 points.

## AUSTRALIAN RESULTS OF 34th A.R.R.L. DX COMPETITION

	C.W. SECTION	Score	Multiplexer	Contacts
VK3EO	...	1,852,900	220	2903
VK3APJ	...	1,371,411	190	2132
VK3AKK	...	828,378	186	1129
VK3FM	...	274,701	127	721
VK4FH	...	222,597	117	637
VK3VN	...	140,784	113	419
VK3FH	...	100,323	84	320
VK3QM	...	68,100	60	454
VK3AND	...	30,913	55	185
VK3KO	...	4,890	33	50
VK3QV	...	3,940	30	65
VK3APJ* (VK3 AFN, OF, QK)	...	178,780	105	571
VK3GN	...	353,376	136	978

### PHONE SECTION

VK3APK	...	1,122,050	158	2075
VK3ATN	...	1,074,780	210	1708
VK3AKK	...	270,073	121	744
VK3EJ	...	188,340	89	730
VK4FH	...	105,444	87	404
VK3QV	...	104,331	83	419
VK3WO	...	33,364	48	331
VK3SM	...	11,828	33	187
VK3FU* (VK3 FU, 23KCM)	...	2,260,718	219	1455
VK3AND* (Multi-op.)	...	180,888	104	898
VK3GN	...	855,869	170	1388

\* Denotes multi-operator stations.

† Denotes Oceania champions.

N.B.—Rules for the 1959 Contest are as for 1958. See page 19 of Jan. 1959 "A.R."


Closing date for logs is 21st April, 1960, and the Contest dates are given in the Contest Calendar.

## AUSTRALIAN RESULTS OF 1958 WPX SSB CONTEST

Call	Band	Score	Contacts	Multiplex
VK3AND	A	119,973	472	87
VK3APK	14	587,418	361	203
VK3FU	7	12,056	89	54
VK3QV	28	41,454	236	63
VK3SM	23	30,195	181	61
VK4FH	A	122,597	453	92
VK3EJ	A	8,300	60	80
VK3LC	14	23,200	128	80
VK3RU	A	217,600	682	100
VK3GN*	A	1,285,842	1787	244
VK3EJ	A	133,085	369	133

\* Winner of KW6JF Trophy for highest Oceania single operator all-band classification.

# AIR-WOUND INDUCTANCES

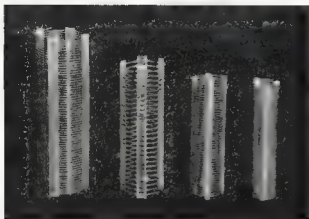

No.	Diam.	Turns per inch	Length	B. & W. Equiv.	Price
1-08	1/2"	8	3"	No. 3002	66c
1-16	1/2"	16	3"	No. 3003	66c
2-08	5/8"	8	3"	No. 3006	76c
2-16	5/8"	16	3"	No. 3007	76c
3-08	3/4"	8	3"	No. 3010	91c
3-16	3/4"	16	3"	No. 3011	91c
4-08	1"	8	3"	No. 3014	\$1.04
4-16	1"	16	3"	No. 3015	\$1.04
5-08	1 1/4"	8	4"	No. 3018	\$1.28
5-16	1 1/4"	16	4"	No. 3019	\$1.28
8-10	2"	10	4"	No. 3907	\$1.68

## SPECIAL ANTENNA ALL-BAND TUNER INDUCTANCE

(equivalent to B. & W. No. 3907-7")

7" length, 2" diameter, 10 turns per inch, \$3.00

References: A.R.R.L. Handbook, 1951; "QST," March 1959; "Amateur Radio," December 1959.

Take the hard work out of Coil Winding—use "WILLIS" AIR-WOUND INDUCTANCES

## WILLIAM WILLIS & CO. PTY. LTD.

430 ELIZABETH ST., MELBOURNE, VIC., 3000.

Phone 34-6539



# NEW CALL SIGNS

JUNE-AUGUST, 1968

VK1CG—G. J. Cashion, 51 Ainsworth St., Mawson, 2007.  
VK1FT—J. F. Tiley, 65 Collings St., Pearce, 2007.  
VK1MR—L. Spencer, 7 Macarthur Ave., O'Connor, 2601.  
VK1NW—N. J. Watling, 103 Antill St., Downer.  
VK1UDM—J. R. Messner, 108 Miller St., O'Connor, 2601.  
VK1BW/T—W. J. Dockrill, 65A Briens Rd., Northmead, 2158.  
VK1FW—R. L. Davies, 35 Belford St., Ingleside, 2007.  
VK1A—W. Adams, 62 East St., West Dubbo, 2836.  
VK1U—A. J. Waugh, 4 Astley St., Werrisbee, 2368.  
VK1L—P. R. Gibson, 9 Railway Pde., Eastwood, 2122.  
VK1SE—J. L. Linakat, Sergeants' Mess, R.A.A.F. Base, Bankstown, 2200.  
VK1VK/T—C. R. Coverdale, 18 Sorrell St., Farmgate, 2151.  
VK1AAU—A. J. Ferguson, 30 Dudley St., Fagewood, 2032.  
VK1ACD—R. Shusterin, 18 Stirling Cres., Lilli Pilli, 2269.  
VK1AWF—B. J. Foster, "Avoca," Bella, via Gunning, 2261.  
VK1AYH—A. H. Howie, 8 Kembla Ave., Chester Hill, 2269.  
VK1BAN—R. R. Pisan, 80 The Kingsway, Cronulla, 2230.  
VK1BAV—B. Nicholson, 33 Valencia Ave., Lugarno, 2210.  
VK1BAU—K. Woodward, 25/26 Morehead St., Redfern, 2018.  
VK1BEL—B. Nicholson, 80 Pringle Ave., Bankstown, 2200.  
VK1BGA—G. A. Alkins, 63 Wambon St., GOSFORD, 2255.  
VK1BGO—G. E. Sheeran, 7 Albion Ave., Pymble, 2072.  
VK1BBO—J. R. Hodgkinson, 11 Burge Pl., Warfield, 2229.  
VK1BIY—B. B. Jones, 22 Armarna Pde., Roseville, 2068.  
VK1BIS—J. L. Davis, 33 Roger St., Lakemba, 2195.  
VK1BMA—Macquarie Radio Club, Station: 160 Bayside, Dubbo, 2830; Postal: Lot A, Warialla Rd., Wongahbat, 2742.  
VK1BMP—P. F. Morrow, 81 Benselong Rd., Crenmore, 2140.  
VK1BMY—J. Vevers, 46 Haig St., Wentworthville, 2145.  
VK1BBA—R. D. Avery, 2 Northcote Rd., Waitara, 2163.  
VK1BBO—G. Gibson, 143 Connela Point Rd., South Hurstville, 2221.  
VK1BBS—R. D. Stephenson, 20A Clouster St., Epping, 2121.  
VK1BSM—D. T. Marr, 69 Brand St., Dundas, 2117.  
VK1BTV—G. G. Turner, 32 Railway St., Wentworthville, 2122.  
VK1BAU—J. L. Edwards, 28 West Ave., Cessnock, 2255.  
VK1BAV—D. J. Allen, 56 Wardell Rd., Peterborough, 2242.  
VK1BAC—C. B. Dein, 21 Barrens St., Strathfeld, 2132.  
VK1BVB—W. S. O'Donnell, 5/14 Victoria Ave., Chateauwood, 2007.  
VK1BCC—A. Pollock, 15 Matthew Pde., Blacktown, 2061.  
VK1BCK—C. W. Harrison, 6 Neerim Ave., Kotara South, 2288.  
VK1BGL—F. C. Kloppenborg, 6/185 Lakemba St., Lakemba, 2195.  
VK1BHM—J. H. Mitchell, 30 Murrumbidgee, Towradgi, 2218.  
VK1BIS—L. B. Miller, 77 Rec Cres., Kotara South, 2288.  
VK1BOE—P. W. Bowers, 28 Thorne St., Wagga Wagga, 2650.  
VK1BPA—L. R. Payne, 19 Seamans Ave., Speers Point, 2264.  
VK1BTG—K. W. Close, C/o Central School, Walgett, 2265.  
VK1BVE—B. J. Evans, 1/148 Kurraha Rd., Neutral Bay, 2089.  
VK1BWW—D. R. Ashton, 1 Headland Rd., Dee Why, 2099.  
VK1BXY—D. J. Barrett, 85 Killikent St., East St. Ives, 2078.  
VK1BZZ—J. F. Cross, 1 Wales St., Charlestown, 2260.  
VK1BI—J. L. Cartmill, 4 Elwood St., Kenmore, 4028.  
VK1APV—P. E. Barker, M.E. 1205, DU DU Rd., Nambour, 4500.  
VK1QV—D. H. Lane, 14 Furdham St., Wavell Heights, 4032.

VK1GE—S. S. St. George, 13 Murray St., Rockhampton, 4700.  
VK1UG—D. J. Richards, 12A Savannah St., Redcliffe, 4030.  
VK1VV—Wireless Institute of Australia, Station: Mt. Mowbray; Postal: G.P.O. Box 639, Brisbane, 4001.  
VK1WR—W. M. Ryan, 72 Netherston St., Nambour, 4500.  
VK1ZC—R. E. Richards, 263 Gold Coast Highway, Palm Beach, 4221.  
VK1ZGT—G. T. Ryan, 95 Railway Pde., Norman Park, 4170.  
VK1ZK—R. K. Adams, 83 High St., Rockhampton, 4700.  
VK1ZRO—E. Robinson, Station: Menno's Rd., Midvale, via Ayr; Postal: P.O. Box 481, Ayr, 4007.  
VK1ZSR—G. R. Sallaway, 14 Gordon St., Hawthorne, 4171.  
VK1ZVZ—J. Richards-Smith, Flat 1, 5 Woolcock St., Red Hill, 4059.  
VK1SA—A. M. Miers, 13 Hill St., Seaford Park, 5649.  
VK1CI—M. S. Lang, Station C, Hall and Primrose Sts., McLaren Vale, 5171.  
VK1PT—P. O. Box 46, McLaren Vale, 5171.  
VK1JZ—W. B. Johnson, 10 Hutton St., Vale Park, 5081.  
VK1JD/T—G. R. Pope, 81 Leabrook Dr., Rosebud, 5073.  
VK1SO—L. N. Allen, 2 Nestor St., Hillcrest, 5098.  
VK1SUC—W. B. R. Brooks, 22 Catherine St., Clapham, 5098.  
VK1SVL—A. M. Voskuken, 26 Bakewell Rd., Evandale, 5098.  
VK1ZBG—O. J. Hambling, 39 Hobart Rd., Hendon, 5003.  
VK1ZDN—P. J. Leonard, 53 Scott Ave., Flinders Park, 5023.  
VK1ZEU—N. G. Scott, 38 Ann St., Ballaburgh, 5023.  
VK1ZFE—N. H. E. Werle, 39 Farmer St., Barmera, 5345.  
VK1ZIB—K. R. Zietz, 13 Fourth Ave., Everard Park, 5033.  
VK1ZRE—O. W. Zinckle, 30 Drysdale Cres., Campbelltown, 5074.  
VK1ZWR—W. R. Chapman, 30 Hatch St., Nurioolpa, 5255.  
VK1ZXX—C. J. Heath, 3 Rutland Ave., Brighton, 5248.  
VK1SAT—C. A. Page, The Rectory, Gnowangup, 5232.  
VK1BI—W. R. Ince, 268 Robinson Ave., Cloverdale, 5105.  
VK1CB—C. E. Berg, 160 Canning H'way, South Perth, 6151.  
VK1CH—J. C. Hulse, 135 Wordsworth Ave., Perth, 6003.  
VK1DM—D. M. McGlinsey, Station: U.S. Navy Command, Exmouth, 6707; Postal: P.O. Box 29, Exmouth, 6707.  
VK1DX—D. L. Smithdale, 87 Cotherstone Rd., Kalamunda, 6078.  
VK1KM—K. M. Moore, 181 Ninth Ave., Ingleside, 6003.  
VK1KR—R. K. Philistom, U.S. Navcomsta, Exmouth, 6707.  
VK1ZGM—E. B. McAndrew, 2 Denby St., Doubleview, 6018.  
VK1ZRR—K. E. Reeves, 5 Allen St., South Perth, 6151.  
VK1CM—C. H. Wall, Professional Officer's Quarters, Darwin Hospital, Darwin, 5780.  
VK1AR—J. R. McCarthy, Station: Aboard delta yachi "Pandemonium"; Postal: C/o P.O. Port Moresby, P.O. Buchanan, Station House 14, 8th St., Lae, N.G.; Postal: P.O. Box 123, Lae, N.G.  
VK1DY—A. T. G. Hanson, Station: Minli Ave., Section 4, Lot 3, Boroko, P.; Postal: P.O. Box 1373, Boroko, P.

VK1MD—R. Drinkrow, Station June Valley, Port Moresby, P. Station: C/o. Box 1144, Boroko, P.  
VK1RD—R. Doty, Station Nukui Village, Stani, South Bougainville, N.G.; Postal: Landmark Baptist College, via Koroia, Free Bougainville, N.G.  
VK1VG—W. Ven Galen, Station: No. 58, Boukai, P., N.G.; Postal: P.O. Box 723, Lae, N.G.

## CANCELLATIONS

VK1RS—R. D. Stephenson, Now VK1BS.  
VK1TW—T. E. Woolley, Now VK1BT.  
VK1WB—W. B. Brooks, Now VK1BC.  
VK1ZCG—J. Cashion, Now VK1CG.  
VK1ZGX—P. G. Bruer, Transferred Interstate.  
VK1ZV—B. Jones, Now VK1BY.  
VK1ZRX—J. F. Tiley, Now VK1FT.  
VK1ZB—H. E. Davies, Now VK1ZC.  
VK1ZDT—A. R. Harrison, Deceased.  
VK1ZG—E. Barlow, Deceased.  
VK1ZOE—W. M. Alworth, Deceased.  
VK1ZES—R. W. Chaplin, Now VK1ZEV.  
VK1ZFB—A. R. Smith, Deceased.  
VK1ZWL—R. Hodge, Now VK1WL.  
VK1ZJ—F. Broome, Now VK1JL.  
VK1ZAC—G. Cochrane, Now VK1ZC.  
VK1ZAT—W. Marks, Transferred Interstate.  
VK1ZAT—Kogarah Evening College Radio Club, Now VK1ZC.  
VK1ZAF—R. McIntosh, Deceased.  
VK1ZAL—T. D. E. Law, Overseas.  
VK1ZAU—M. G. Burleigh, Now VK1JU.  
VK1ZAD/T—R. B. McPhie, Now VK1ZC.  
VK1ZAT—J. F. Dockrill, Now VK1BW/T.  
VK1ZAV—W. Rogers, Transferred to U.S.A.  
VK1ZAW—N. J. Watling, Now VK1NW.  
VK1ZB—F. B. Crum, Overseas.  
VK1ZBA—Boy Scouts' Assoc. (N.S.W. Branch), Now VK1BA.  
VK1ZAU—K. Woodward, Now VK1BAU.  
VK1ZB—R. D. Avery, Now VK1BBA.  
VK1ZCM—J. Linden, Transferred Interstate.  
VK1ZCB—A. W. Sullivan, Now VK1BAS.  
VK1ZCD—J. F. Dockrill, Now VK1BW/T.  
VK1ZEX—G. D. L. Armstrong, Now VK1ZEV.  
VK1ZEE—A. A. Campbell, Now VK1ZC.  
VK1ZHK—J. P. Hodgkinson, Now VK1BHO.  
VK1ZIO—A. J. Waugh, Now VK1BI.  
VK1ZKK—K. J. Callaghan, Now VK1ZC.  
VK1ZNV—M. F. Vevers, Now VK1BMY.  
VK1ZBN—R. L. Davies, Now VK1BTV.  
VK1ZSN—R. Shusterin, Now VK1ACD.  
VK1ZTB—G. Gibson, Now VK1BBO.  
VK1ZTR—R. Turner, Now VK1BTV.  
VK1ZUF—J. Ford, Now VK1ZC.  
VK1ZVL—K. Laws, Now VK1BKL.  
VK1ZV—J. M. Shaw, Transferred to Victoria.  
VK1ZV—P. Kempster, Cashed operation.  
VK1ZV—J. F. Sawford, Deceased.  
VK1ZAP/T—R. R. Pope, Now VK1JD/T.  
VK1ZB—J. M. Shaw, Transferred to Victoria.  
VK1ZIK—D. W. Carr, Cashed operation.  
VK1ZKN—K. Kohler, Now VK1ZDV.  
VK1ZUL—A. M. Voskuken, Now VK1SVL.  
VK1ZB—D. B. O'Brien, Now VK1ZC.  
VK1ZSG—S. S. St. George, Now VK1GE.  
VK1ZAB—H. Hilla, Now VK1ZC.  
VK1ZBK—K. Moore, Now VK1KCM.  
VK1ZCC—M. L. O'Rourke, Now VK1ZC.  
VK1ZEM—B. M. McDonald, Cashed operation.  
VK1ZFB—R. Campbell, Leaving to Gland.  
VK1ZGK—P. C. Kloppenborg, Now VK1ZGL.  
VK1ZAD—A. M. Miers, Now VK1SA.  
VK1ZAU—D. Tanner, Now VK1AAU.  
VK1ZL—L. Lane, Now VK1QV.  
VK1ZAG—G. A. Nunn, Transferred to Victoria.  
VK1ZGW—G. K. Williamson, Now VK1ZC.  
VK1ZJ—J. C. Lee, Transferred to Gland.  
VK1ZJ—J. Wirth, Transferred to Nauru.  
VK1ZGW—W. Van Galen, Now VK1VG.

## For Reliable Connections



RESIN CORE SOLDERS

O. T. LEMPIERRE & CO. LIMITED

Head Office: 21-41 Bourke St., Alexandria, N.S.W., 2015 and at Melbourne, Brisbane, Adelaide, Perth, Newcastle

OT/70



# THE QUESTIONNAIRE—A PROGRESS REPORT

All replies received up to and including 24th December have been taken into account. The final returns were better than we had really expected, the returns representing 30.3% of our circulation. The individual State results were:

VK1-2 26.8%	VK5-8 30.8%
VK3 37.3%	VK6 27.25%
VK4-9 35.9%	VK7 28.6%

In addition, replies were received from U.S.A. and New Zealand.

We believe we have a fairly accurate cross-section of the Amateur ranks and interests, so feel reasonably confident that the figures we will produce will be an accurate indication of our readers' interests. At this time we have not processed the answers to all the questions, hence our report will be spread over several issues.

## MONEY SPENT

During the last two years the breakdown of money spent shows:

29.3% spent less than \$100.
28.2% spent between \$100 & \$200.
12.7% spent between \$200 & \$300.
6.32% spent between \$300 & \$400.
6.18% spent between \$400 & \$500.
4.8% spent between \$500 & \$600.
11.75% spent over \$600.

Just on 1.5% did not answer this question.

In order to make an estimate of what money is spent on Amateur Radio per year, we took the middle figure of each range, i.e. \$150, for \$100 to \$200 range, etc., but this left us with the problem of what to use as a realistic figure for those in the "over \$600" bracket. We, therefore, spoke to a few of those who had spent over \$600 and asked what they estimated they had spent. From their replies we estimated that \$850 would be a fair average, so used this figure in our calculations. On these figures we estimate that Amateurs are spending in the vicinity of \$560,000 per year in Australia, or an average of \$132 each.

The State averages came to:

VK1-2 \$131	VK5-8 \$108½
VK3 \$132½	VK6 \$185
VK4-9 \$147½	VK7 \$138

Indications are that the spending will be much the same over the next couple of years as to the question on future spending, 41.7% said they would spend the same, 28.4% will spend more, and 28.4% less. When broken down into brackets, we get future spending as follows:

	Spent Same	Spent More	Spent Less
Under \$100	47.0%	42.5%	10.5%
\$100-\$200	52.5%	33.8%	13.7%
\$200-\$300	35.5%	34.0%	30.5%
\$300-\$400	37.0%	16.1%	48.9%
\$400-\$500	38.0%	18.5%	45.5%
\$500-\$600	35.2%	—	64.8%
Over \$600	26.3%	5.75%	67.0%

Although we did not ask what those contemplating extra spending had programmed, quite a number indicated what they had in mind and comments

such as "going s.s.b." and "contemplating a transceiver" were frequent. We hope that at a later date to find time to analyse the future spending on a "per State" basis.

## TYPE OF EQUIPMENT

On the subject of type of equipment, 53.2% are mainly "home-brew", 38.6% mainly commercial, and 18.2% reported 50/50. The findings on a State by State basis are:

	Home-Brew	Commercial	50/50
VK1-3	51.0%	30.5%	18.5%
VK3	52.0%	34.2%	13.8%
VK4-9	48.5%	32.3%	19.2%
VK5-8	70.4%	18.3%	17.3%
VK6	49.5%	39.2%	11.3%
VK7	65.8%	20.7%	13.4%

Undoubtedly the high percentage of commercial gear in VK6 accounts for their high "per capita" spending, and by the same token the small percentage of commercial gear in VK5 explains their low per capita expenditure. It would be interesting to know why VK5 and VK7 have so much more home-brew equipment than the other States, and we hope this may be revealed as we analyse the figures on operating modes and bands.

## ADVERTISING SPACE

The question regarding what space should be allocated to advertising presented the main problem. Where two amounts were ringed, we have taken the higher figure. Those who wrote such comments as "as much as you can get", etc., have been listed as no opinion, giving the following results:

20% advertising space	8.2%
30% " "	33.0%
40% " "	24.8%
50% " "	16.7%
60% " "	7.6%
No opinion	9.9%

The State by State voting was reasonably even as the following table shows:

	VK	VK3	VK4-9	VK5	VK6	VK7
Space 1-2	9.7	7.75	7.9	7.0	4.5	12.0
30%	32.8	31.4	31.8	35.5	41.0	30.0
40%	23.8	25.0	25.2	24.4	26.8	26.9
50%	16.25	16.5	18.8	16.3	8.9	17.9
60%	8.9	7.5	8.0	8.75	5.5	6.0
No opinion	8.7	11.8	9.0	8.1	13.3	7.2

These findings confirm our opinion that 30% to 40% of space allocation to advertising was what the majority wanted, and this was the range we have aimed at in previous years. This is contrary to the policy of most magazines which appear to aim at a figure between 60% and 70%. How long we can maintain the lower space allocation is a matter of economics and the final decision cannot be reached until we know what we are going to get for the magazine after our new approach for a price increase is considered at Easter next.

## EMPLOYMENT IN THE ELECTRONICS INDUSTRY

To wind up this month's progress report we shall briefly cover the matter of employment in the electronics industry. The national average is 38.8%. Again the States show fairly consistent figures as can be seen from the following table:

VK1-2 44.25%	VK5-8 36.6%
VK3 35.4%	VK6 44.5%
VK4-9 34.7%	VK7 37.4%

We should mention the reason for grouping certain call areas together is to conform with our circulation figures which are grouped the same way.

Next month we will deal with the readers' preferences.

★

## VK2 BUSHFIRES

(Continued from Page 17)

Networks were officially closed at Springwood on Friday night and at Penrith on Saturday morning. All members remained on call, however, for several days, but the situation was relieved by rainfall.

A de-briefing was scheduled for 11th December at St. Marys for participating groups to enumerate lessons learnt and enable preparation for the next time to be undertaken.

I feel that the general result of this operation was a wonderful shot in the arm to relations between the Amateur Service and the fire-fighting organisations in N.S.W. The Bushfire Committee Radio Officer, Mr. H. Freeman (VK3BHF), Inspector W. Hodder, the Blue Mountains District Inspector N.S.W. Fire Brigades, the Blue Mountains Fire Control Officer (Mr. B. Dowling) and many others associated with the control centre at Springwood were all very generous in their praise of our efforts.

A lot of the traffic we passed, e.g. fire reports, personnel movements, etc., were duplicates of material passed on other networks, but nevertheless essential in our "back-up" function. However, in many instances the Amateur networks were the primary conveyors of messages and information and the fire controllers soon learnt our value! I also feel that the guys involved require a really good pat on the back for their part in an unrehearsed net operation which proved to be very successful.

Before concluding, let me quote a wise comment from Bill VK3HZ: "It is practically impossible to get a full picture of all activity and assistance rendered by the many Amateurs, some of whom journeyed from Sydney to assist. Everyone was so busy in net operations that an individual story of each Amateur's work could never be recorded. I should only like to thank all those involved for their excellent co-operation and assistance." To these remarks I should like to add my own personal thanks and to say that due largely to my own involvement in this operation I may have done some inaccurate reporting, or omitted a call sign. If I have, please accept my apologies and inform the readers that the residents of the mountains have undergone a severe crisis in recent weeks. We wish to say to all . . . your help was wonderful.

(Acknowledgments to VK3HZ and VK3ZIN who helped me by filling in gaps and with helpful comments, and to VK3GN for additional information.)

★

## CONTEST CALENDAR

1st/16th Feb.—A.R.R.L. Novice Round-up.
15th/18th Feb.—35th A.R.R.L. DX Test (c.w. section, 1st week-end)
1st/2nd Mar.—30th A.R.R.L. DX Test (phone section, 2nd week-end)
8th/9th Mar.—32nd R.E.R.U. Contest (R.S.G.B.)
15th/18th Mar.—35th A.R.R.L. DX Test (c.w. section, 2nd week-end)

D Rankin, VK2QV, F.E.

9F3USA-VZBQ. 9KZHV-WBGR. 9SHIM-KAGGN. 9SMZD-WECUF. DX1IAAV-C/o. American Embassy, A.P.O. San Francisco, U.S.A. 9MMAA-Box 80, Las Palmas, Canary Is. 9MFPF-Box 860, Las Palmas, Canary Is. KAILI Via KRWXV/1, D. Janicki, 161 First Ave., South Portland, Maine, U.S.A., 94196. KV4FZ (ex W0VXO) Box 310, Christmansted, St. Croix, U.S. Virgin Is. M11-Test QSL via Ivo Grandoni, Rep. of San Marino. P00CC-Via WZTA (ex W2ADE), J. Doremus, Pocono Rd., Mountain Lakes, N.J., 07064. VSEDO-V. Bailey, C/o. Police H.Q., Aeronal St., Hong Kong. WBAGCL/Y80-C/o. American Embassy, A.P.O., San Francisco, 95249. YB0AR-Gungunangari 31, Djakarta, Indonesia.

#### ACTIVITIES

The new 58 DXCC Award has certainly given a much needed boost to the ailing sport of DXing. Overcast stations are quite enthusiastic about the award, and there has been plenty of the clean crisp operating that makes DX hunting so enjoyable. To clear up any misapprehensions about the rules, DXCC can be worked on any five Amateur bands. The rules in last month's issue did not make this completely clear.

Reg VK4VX has been slacking up DX after DX in his log book over the past few months. He has averaged more than 60 countries per month on 20 m.c.w.s.a.b. Reg says that conditions are so good at the moment that it should be possible to work 100 countries on 20 m.c.w.s.a.b. within a month. A whole footscape page listing stations worked supports this. The list abounds with DX, perhaps the best being AC3CP at 1044s on c.w. Also one 620AA at 1052s (171).

Al VKAS3 says that 10 m.c.w.s.a.b. is beginning to fall off now, but 15 m.c.w.s.a.b. should remain good for another season or two. Al sent a list of stations worked on 15 m.c.w.s.a.b. and a few on 20 m.c.w.s.a.b. and it appears that most parts of the world are workable on 15 m.c.w.s.a.b. between 6 and 11 p.m. E.A.S.T. The main activity is in the first 30 Kc. Al says that 20 m.c.w.s.a.b. is excellent to South Africa around 17. Can anyone please help with the QRA of 620AA?

Fred VKARF also sent in a huge list of DX worked, all 20 m.c.w.s.a.b. The most apparent feature of the list is the large numbers of African and Middle East stations worked. There are plenty of rare ones, including T0GAB, T0UAY, 4U0TIC and so on. Unfortunately space does not allow us to print the full list, but be assured that now is the time to pick up countries on 20 m.c.w.s.a.b.

George L0043 has been maintaining an almost nightly check on three African c.w.s.a.b. stations, KPH, WNU and WCC, which are just above 2 Mc. The idea behind this investigation has been to see how many times per month these stations could be heard, and use the information to predict openings on 180 m.c.w.s.a.b. George has just completed an analysis covering the last 14 months on the above stations, and a definite pattern emerges showing peak conditions at the equinoxes and a very definite low at our winter solstices. There is a null in our summer solstices as well, but not as low as one would expect. (Evidence of on-way ship? Ed)

George says it is pretty obvious that the short path to W0T on 160 is open quite often and Amateur QSOs would have been possible on a number of dates were it not for the fact that local time there would be around 03/04. Latest heard

Dec. 7-1114-1124s, 1955 Kc. W1RB. " 14-1324-1424s, 1954 Kc. W0RQ, W0GEM (trans-pacific test). " 15-1124-1203s, 1938/4 Kc. W8ANO, " 15-1153-1203s, 1990 Kc. VZ8QU.

#### DXCC AWARD AMENDMENT

(Not 58 DXCC) Issued free of charge to A.R.E.L. members; others remit \$4.00 for DXCC Award, and \$1.00 with each endorsement. In addition, send sufficient postage for return of QSLs, preferably sufficient for 1st class regd. mail.

#### SUMMARY

I would like to thank the gang of ever helpful VKs who keep this column supplied with information. Remember, news is always needed. Acknowledgments to QSL News, L10VW, Z1AD4A, Z1AFZ, O1VGT, V8AS, VKARF, VK4VX and last but not least L0043. Good hunting chaps. 73, Peter VK3APN.

Sub-editor: PETER NEBBIT, VK3APN  
32 The Grange, East Malvern, Vic., 3145  
(All times in GMT)

#### ASSORTED

It is reported that 1 stations will shortly use location prefixes as follows: 11 Special services, 12 Milan, 13 Venice, 14 Bologna, 15 Florence, 16 Bari, 17 Naples, 18 Reggio Calabria, 19 Piedmont, 10 Rome. The islands will remain as ITL, ISL, etc. (Good news for the prefix hunters.)

While on the subject of prefixes, DX1 is a new one that has just been issued. DX1AAV (ex W3TC), who works for the American Embassy in Manila, says that the prefix will be used by visitors to the Philippines. At present there are no others using DX1, but there should be three more on shortly. As yet there is no reciprocal licensing arrangement, but the matter is being looked in to. Larry says he will be there until June. His QSL address is given below.

Erl WAUZEU plans to make a DX-pedition to Chicago, IL, and Monaco next May. He is particularly interested in making contacts with VK/ZLs.

Those OM prefixes that everyone was talking about a couple of months ago were allocated to about 300 OK stations, to celebrate the 50th Anniversary of the Independence of Czechoslovakia. The prefix was due to expire last December—the 16th.

U.K. Amateurs are now permitted to send their call signs at 30 words per minute instead of 12.

VE1AJT/VE5APV DX-pedition: Don and George are reported to have signed /X08 for about a month from Cienfuegos, Cuba, to their departure for K86. Don is said to have plans to link up with K860LU when the latter goes to FWH about 1st Feb for 15 days of operation on all bands including 135 m.c.w.s.a.b. VE2BUJ/SU QSL: VE2NV asks stations not to QSL via the VE3 Bureau, as he has not heard from Gerry for 15 months, and no logs are available.

Malpelo Island, HK0: K4PHY, K4JGS, W4IRA and TICMF are reported to be going there for one week in February.

#### BAND NEWS

Rolf HC8RS is said to operate 21275 s.a.b. daily at 22/24s.

WBAGCL/Y80 is reported QRV since Dec. 12, 1403 s.a.b. daily at 10/15s. QSL information below.

Carole 7G1CG is said to sked WASHUP on 21300-320 s.a.b. about 21s, with WASHUP on earlier to arrange skeds.

Sid 8X2AX is QRV daily 7040 at 0600-0630s. This would be a real challenge for long path; a sked for about 07s might be the best shot.

Z3EM1 Martin, Ix1: Don is generally QRV Mondays/Wednesdays/Fridays about 14180 a.m. at 0300-0330s. He skeds Dennis. Z360P most days 14215 s.a.b. at 04s. If you work Dennis he will arrange a sked for you.

HLRWK Rod (ex W7YX1) is QRV all bands 80-10 m.c.w.s.a.b. He skeds his QSL manager KTCRT on 1415 s.a.b. at 14s. He skeds Suno. QRV for other stations before/after the skeds. Skeds can also be made via KTCRT.

#### QSL MANAGERS

CEBAT-CE3ZN  
CH4LF-W3HINK  
CH4RF-DL7PT  
CT3REL-W3ELF  
F0EXA-FR7ZD  
FM7WV-FJKK  
FM7WV-FR7ZD  
HC8RS-SM5EAC  
HK0BMO-WA0AIF  
HL8WK-KTCRT  
HV3VY-BV3VY  
HV3VY-WK6NL  
JX5CI-LASCL  
K4VFA-K4KXN  
M4M8I-G3FOA  
OY5NS-K1QLT  
P2JMI-VE8EUT  
P3KAZ-SM8BQ  
T4ZEM-W0ADK  
T4ZEM-K4EPL  
T43AB-W1MOT  
T43X-W4YGA  
T73WLN-W43BZO  
T0BRN-DL3RK  
T4JCL-VZ8QU  
T0U2Z-DL7PT  
V7AGBR-W4WES  
VF4VY-KV4EY.

VG3CG-G3APA  
VR1P-VE8AO  
VR1PS-VJ0IS  
V80M-VL3BE  
V86CS-SM2NF  
V86MB-Co3n-W3CTN  
V86MB-John-C3KDB  
V02JA-W3CTN  
XW3CAL-VE8AO  
ZB2AY-K3RLY  
ZB2AY-VL3BE  
ZDRK-WV9VC  
ZDWB-W3HKK  
ZSENI-Z501B  
Z53BS-WB2RL  
Z53LU-W3CTN  
Z40AY-T1ZBS  
Z40AY-DL4WE  
4572D-WF7  
471AD0-HB9AD0.  
5N2AS-G3V  
5UTAN-W4WPH  
5W1AR-W4ZKI  
601GB-W1YRC  
6W4DQ-WM6S  
7X0AR-VZ8QU  
8Q4LK-V3YOLK  
8Q4YL-457UL

## \*AEGIS\*

\*Registered Trade Mark

### QUALITY PRODUCTS

available all radio parts stores



### AF1 Noise Reducing Aerial Kit

For use in noisy locations for clearer reception. Designed to cover both M/W and S/W broadcast bands (from 500 to 1500 Kc. and 2 to 15 Mc. approximately)

Available in All States

## AEGIS PTY. LTD.



Write for Illustrated Knob Leaflet.

347 Darebin Road Thornbury, Vic. 3071  
P O BOX 49, Thornbury, Vic. 3071  
Phones 49-1017, 49-6792

## SILENT KEY

It is with deep regret that we record the passing of the following Amateurs:

VK3CT—R. B. Pinning.  
VK3GZ—Max Folie.

## FEDERAL QSL BUREAU

Latest details on the proposed DX-Exemption to Norfolk Island and Cocos-Keeling Islands by Jack Snyner, W8PO, and Bob James, W4WS (ex W4CHA), indicate they will arrive in Sydney on 24th February and will be operating from Norfolk for two days from 12th February. They are scheduled to arrive in Perth about 24th Feb and at Cocos on 26th Feb. Owing to the infrequent air schedules to Cocos (every three weeks) it is not certain that Jack will be able to make the Cocos trip but he must be back on his job early in March, but Bob, who is retired, will definitely make the Cocos location. The Cocos operation will last for three weeks. At both venues, Jack will sign VK3BPO and Bob will sign VK3BPR/2.

A visitor to Australia early in March will be K3KA. His schedule provides a stay in Melbourne from 28th Feb. to 3rd March. Information on his movements may be obtained from either VK3AKB or VK3TE. He may be operative from Norfolk Island under the call sign VK3KA.

A new award sponsored by the Gaurcho Radio Club, Brazil, is called the C-30-B Award. Information on the requirements may be obtained from this Bureau.

The National Amateur Radio Union of Greece has issued a new award. They have set details of the requirements which may be obtained from this Bureau.

REF member, S.W. F12908, Pierre Galtier, Box X, Vinux Fort, 49 Vincennes, again complains that VK stations will not QSL even when he includes an I.R.C. He lists 13 VK stations who have converted his I.R.C. to other use. What about it fellows, no matter what your views on S.W. reports it is dishonest and discourteous to ignore an I.R.C. report. If your cards are too costly to "waste" on S.W.s, reply on a piece of paper.

Bruno, KBQOQ, who worked in VK for a few years back, has now migrated to VK. He reached Melbourne with a 10,000 lower in 4th January. Bruno, wisely, would prefer to settle in Melbourne, but employment opportunities in the electronics field are greater in Sydney, so it appears that Sydney will be his permanent location.

Bureau statistics for the year 1968 show a total of 41,574 cards handled. This compares with 38,234 in 1967 and 78,453 in 1966. The Bureau would have been 10,000 lower if the Russians had observed the new arrangements earlier than October. At long last am getting a breather!

"Qs" from July 1967 to May 1968 inclusive are available gratis on personal application at this Bureau. First up best dressed and no phone reservations. Good hunting, good health and good QSL results in 1969.

—Ray Jones, VK3BJJ, Manager.

## REPAIRS TO RECEIVERS, TRANSMITTERS

Constructing and testing: xtal conv., any frequency; Q5-ers, R9-ers, and transistorised equipment.

## ECCLESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 30-3777

## Stockists of Radio and Electronic Components for the Amateur Constructor and Hobbyist

First Ring, Write or Call on

**WILLIAM WILLIS** & Co. Pty. Ltd.

430 Elizabeth St., Melbourne. Ph. 34-6339

## Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the Publishers.

### REMEMBRANCE DAY CONTEST

Editor "A.R.," Dear Sir,

I have a bone to chew over about the Remembrance Day Contest. It was stated in the results for 1968 in the November issue that "VK3DK's tally of 1823 points for 18 1/2 hours of operating could stand as a record for some time". Evidently this statement was made having done no research into the results of previous contests or that the points obtained for Amateurs in VK0, VK1, VK3 and VK33 mean nothing and don't count.

On going back through previous results to 1960, I find that this score has been exceeded by two Amateurs, VK0WH 3220 points in 1960, and VK0CR 2078 points in 1967, so how can Den's commendable result be still considered a record? I think for the first time the 2000 point mark was broken last year.

I had not really thought about the rules for the R.D. Contest before the above inaccuracy appeared, but now feel on reflecting that the contest treats those in the VK0, VK1, VK3 and VK33 areas as the ugly ducklings. Surely these scattered Amateurs in these areas could be treated for the purpose of such a contest as a separate division and as such eligible for award of the trophy should results indicate so. I imagine quite a number of the chaps in these areas are members of the W.I.A. or various Divisions. I think there were points for percentage of Amateurs participating for 1967 and 1968 I feel sure Antarcica would win hands down with a 99% participation rate.

What about it chaps? Aren't these outlying Amateurs who give us so much of our interesting DX work consideration as regards our own domestic contest? I definitely think so, what say you?

—Rodney Chapman, VK3UG.

### ERRORS IN R.D. CONTEST RESULTS

Editor "A.R.," Dear Sir,

Regarding the R.D. Contest results, I believe an error has crept in. The station VK3ASW/P is shown in the open section with 1063 points. It should, I think, read VK3AFW/P as I operated this station (VK3AFW/P) and claimed 1063 points for the "open" section and my call sign elsewhere. It appears that there is a misprint or a strange co-incidence.

—R. R. Cook, VK3AFW.

Editor "A.R.," Dear Sir,

It appears that in the R.D. results, page 11, November issue, a small mistake has been made. Instead of VK3ZL as top VK1 c.w. score, it should read VK3TE. I don't think there is a VK3ZL but I can't find a postal address. I deny the inference that I used a 10kW, b.c. transmitter in the contest, hi, hi! I am sure this is correct as the points score is the same as I claimed.

—Mike Jenner, VK3TFB.

## Wireless Institute of Australia

### Victorian Division

## AOC CLASS

Morse:

THURSDAY, 6th FEB., 1969

Theory:

TUESDAY, 18th FEB., 1969

Theory is held on Tuesday evenings, and Morse and Regulations on Thursday evenings, 8 to 10 p.m.

Persons desirous of being enrolled should communicate with Secretary W.I.A., Victorian Division, P.O. Box 36, East Melbourne, Vic., 3002 (Phone 41-3535, 10 a.m. to 3 p.m.)

## PAINTON TECHNICAL DATA

A series of technical leaflets and brochures on a range of connectors, resistors, switches, r.f. chokes and a variety of other components is available from Painton (Australia) Pty. Ltd. Readers are asked to note Painton's new address: Painton (Aust.) Pty. Ltd., 29 Railway Ave., Huntingdale, Vic., 3166. Phone 569-0831.

## HAMADS

Minimum \$1 for forty words.

Extra words, 3 cents each.

HAMADS WILL NOT BE PUBLISHED UNLESS ACCOMPANIED BY REMITTANCE.

Advertisements under this heading will be accepted only from Amateurs in S.A.W. Stations reserve the right to reject any advertising which, in their opinion, is of a commercial nature. Copy must be received at P.O. 36, East Melbourne, Vic., 3002, by 4th of the month, and remittance must accompany the advertisement.

**COLLINS** S-line 758-3S Receiver, 329-3 Transmitter, 518F-2 Power Supply, perfect condition. Cost \$2,500, will sell for \$1,100. Hints, complete with cables, microphone, speaker and 240v./115v. transformer. Also for sale Heath HA-14 Linear Amplifier, 875. Newtronics 10-80 mc. Var-tical, 320. VICIADP, Ray Shurman, Birling Gass, Lilli Pitt, N.S.W., 2229. Tel. 524-3893

**FOR SALE** Eico 753 Transceiver, s.a.b.-s.m.-w., 30-40-20 180w. p.p., complete with ceramic p.t.t., microphone, perfect condition. \$165. Power supply available if required. 853. ARCS Command Receiver, EC453, 12v. heaters, extra audio stage, 3.5 ohm speaker, 400 ohm re-bal. front panel gain, a.f. gain, b.f.o. switch, bezel, 50 ohm spiral input, new condition. \$20. Les Diner, VK3NU, 3 Cowrie St., Torrens Park, S.A., 5022. Tel. 70-8608.

**FOR SALE** Heath 58-400 s.a.b., 5-band Transmitter. Built-in o.e.p.s., vox, etc. Clean condition. Performance well. 3225 o.n.o. W. J. Bell, VK3WK, Warrnambool, Vic., 3279. Phone Gramsme 84-2225

**FOR SALE** Pelag Valve and Circuit Tester, 520 o.n.o. 0-1 mA. Meter, 4 in. diam. with multimeter scale, 3, 0-100 mA. 3 in. diam. Weston, 83. Five 455 Kc. crystals, \$2.50 lot. W. R. Jardine, P.O. Box 65, Leongatha, Vic., 3653

**SALE** First \$50 dollar bank cheque taken Swan 350 with matching power supply, upper, lower slidebanks, latest crystal filter, full 10 metre coverage, mic. unpaired, serial cert. 10. V2K warrt VK20T P.O. Box 20, Goolburn, N.S.W., 2560.

**SELL** FL200B Transmitter, F100B Receiver, crystal mic, speaker, i.f. kit, cables, etc. xtal calibrator, 100 mc. unpaired, serial cert. 10. 10. readout. 8555 o.n.o. Tel. 379-5468 [Melo]

**SELL** Galvy V., as new manual, circuit, some spare tubes. \$400. Channel Master Audio Router, complete, full race thru filter, new, in carton, 350. Two identical AVA boards, 5288 kc. carrier scale, for use base transceiver or cascade. \$25. Pair Philips CR3-330 tubes, bases, 810. Bend's Compass Kit, professionally improved, s.m., s.a.b. with 20 mx and 15 mx xtal converters, built-in p.s., \$40 o.n.o. A.W.A. xtal calibrator, 1 m. cert. 10. V2K Kc. in-built p.s., \$10. 1155 Rc. front-end and i.f. goes, bettered, 87 D Fisher, P.O. Box 33, Depto, N.S.W. 2530. Phone Wollongong 61-2144.













**SELL** Swan Transceiver complete with vox, p.t.t., a.i.c., 240v. a.c. and 12v. d.c. power supplies, connecting cords and speaker, full coverage 60, 40 and 20 mc. bands \$350. VK4XQ, G. D. Down, 37 Geraldine St., Ervinton Park, Brisbane, Qld., 4253.

**SELL** 51483 Brand new 5146 valves, in cartons, only \$2.50 each plus postage. Remittance with order to VK6WJ, J. Pollock, 15 Matthew Pde., Blackland N.S.W. 2774. Phone Glarbrook 7-1523

**WANTED TO BUY** AR7 Communications Receiver, or similar. Must be complete, \$40 to \$80 With power supply. State price and condition. Reply to D. Harrison, P.M.B. Khamboon, via Corrang, Vic. 3707. Phone Khamboon 5403.
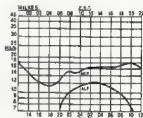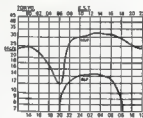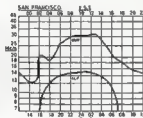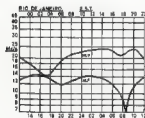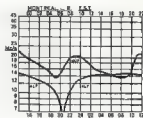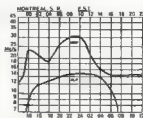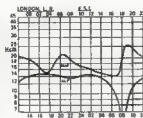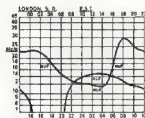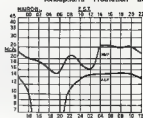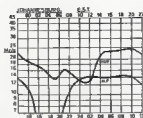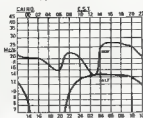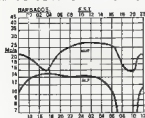
# PREDICTION CHARTS FOR FEBRUARY 1969

(Prediction Charts by courtesy of Ionospheric Prediction Service)



## GELOSO AMATEUR-BAND TRANSMITTER

### Model G4/225

A complete Transmitter that gives an Amateur all the facilities for modern communications for CW, SSB, DSB, and AM modes.

#### FEATURING—

- ★ Crystal stabilised VFO.
- ★ 160-200 watts PEP on SSB.
- ★ 80 metres through to 10 metres.
- ★ 16 tubes with a pair of 6146s in PA.
- ★ 100% AM modulation.
- ★ Break-in keying for CW.
- ★ VOX operation.
- ★ Netting switch.
- ★ PI coupler output.
- ★ Modulation meter incorporated.



GELOSO Transmitters, Receivers and VFOs have been marketed in Australia for over 15 years with complete success.

A companion Receiver to the G4/225 is the G4/216. Both are available from stock.

Available direct  
from Australian  
Agents:

**R.H. Cunningham**  
PTY. LTD.

Send for Technical Bulletin No. 96 for complete information and details.

HAM PRICE: G4/225 Transmitter, \$310.00 plus sales tax.  
G4/226 Power Supply, \$124.50 plus sales tax

608 COLLINS STREET, MELBOURNE, VIC., 3000  
Telephone 61-2464

64 ALFRED ST., MILSONS POINT, N.S.W., 2061  
Telephone 929-8066

# radioparts

PROPRIETARY LIMITED

## CUSTOMER SERVICE



## 'RAPAR' MULTI-TESTER

MODEL YT 68A  
MULTIMETER

Pocket Size: 2.4" x 3.3" x 1.2".

### SPECIFICATIONS:

DC Voltage: 0 to 10, 50, 250, 1,000V.

AC Voltage: 0 to 10, 250, 500V.

DC Current: 0 to 250 mA.

Resistance: 0 to 100K.

Battery: 1.5V. (1 x 915).

Weight: about 7 oz.

A powerful magnet is mounted on the back of the case which enables the instrument to adhere to all steel surfaces.

The tester has a meter sensitivity of 1,000 O.P.V.

**\$9.00** including tax



## RADIO PARTS PTY. LTD.

MELBOURNE'S WHOLESALE HOUSE

562 Spencer St., Melbourne, Vic., 3000. Phone 329-7888, Orders 30-2224

City Depot: 157 Elizabeth Street, Melbourne, Vic., 3000. Phone 67-2699

Southern Depot: 1103 Dandenong Rd., East Malvern, Vic., 3145. Ph. 211-6921

**OPEN SATURDAY MORNINGS!**

# TRIO

## communications receivers and transceivers



MODEL 9R-59DE

**COMMUNICATIONS & AMATEUR RECEIVER**

(WITH MECHANICAL FILTERS)

### SPECIFICATIONS:

**FREQUENCY RANGE:** Band A—550-1,600 Kcs.; Band B—1.6-4.8 Mcs.; Band C—4.8-14.5 Mcs.; Band D—10.5-30 Mcs.

**BANDSPREAD:** Calibrated Electrical Bandspread, 80 and 40 metres—5 Kcs. per division, 20 and 15 metres—10 Kcs. per division, 10 metres—50 Kcs. per division.

**ANTENNA INPUT:** 50-400 ohms impedance.

**AUDIO POWER OUTPUT:** 1.5 watts.

**SENSITIVITY:** 2 $\mu$ V for 10 dB S/N Ratio (at 10 Mcs.).

**SELECTIVITY:**  $\pm 5$  Kcs. at -40 dB ( $\pm 1.3$  Kcs. at -4 dB). When using the Mechanical Filter.

**BFO FREQUENCY:** 405 Kcs.  $\pm 2.5$  Kcs.

**SPEAKER OUTPUT:** 4 or 8 ohms.

**HEADPHONE OUTPUT:** Low impedance.

**TUBE COMPLEMENT:** V1—6BA6 RF Amplifier; V2—6BE6 Mixer; V3—6AQ5 HF Oscillator; V4—6BA6 1st IF Amplifier; V5—6BA6 2nd IF Amplifier; V6—6BE6 Product Detector; V7—6AQ5 Beat Frequency Oscillator; V8—6AQ5 1st AF Amplifier; V9—6AQ5 Audio Output; 1N40-AF Detector; 1N40, 5W-65—AVC; 5W-65—AHL; 5W-65 x 2—Rectifiers. \$175.00 FOR/FOA SYDNEY

MODEL JR-500SE

**AMATEUR BAND COMMUNICATIONS RECEIVER**



### SPECIFICATIONS:

**FREQUENCY RANGE:** 80 Meters 3.5-4.0 Mcs.; 40 Meters 7.0-7.5 Mcs.; 20 Meters 14.0-14.5 Mcs.; 15 Meters 21.0-21.5 Mcs.; 10 Meters 28.0-28.5 Mcs.; 10 Meters 28.5-29.1 Mcs.; 10 Meters 29.1-29.7 Mcs.

**MODE:** AM, Single Sideband and CW.

**SELECTIVITY:** Band width  $\pm 2$  Kcs. at 6 dB down,  $\pm 4$  Kcs. at 40 dB down. Uses Mechanical Filter. Sensitivity: Less than 1.5 microvolts for 10 dB signal to noise ratio.

**SPIRIOUS RESPONSES:** Image rejection more than 40 dB IF rejection more than 40 dB.

**AUDIO OUTPUT:** 1 watt maximum.

**TUBE COMPLEMENT:** V1—6BE6 RF Amplifier; V2—6BE6 Crystal controlled 1st mixer; V3—6BE6 2nd mixer; V4—6BA6 IF amplifier; V5—6BA6 IF amplifier; V6—6AQ5 BFO and product detector; V7—6BA6 Audio amplifier.

**TRANSISTORS:** Q1—2SC185 Buffer; Q2—2SC185 VFO. \$282.30 FOR/FOA SYDNEY

CONSULT YOUR LOCAL RADIO DEALER, OR

MAIL THIS COUPON *today*

Please forward free illustrated literature and specifications on Trio equipment.

Name \_\_\_\_\_

Address \_\_\_\_\_



(A unit of Jacoby Mitchell Holdings Ltd.)  
376 EASTERN VALLEY WAY, ROSEVILLE, N.E.W.  
Cables and Telegraphic Address: 'WESTELEC',  
Sydney, Phone: 40 1212

# LOW DRIFT CRYSTALS

★

1.6 Mc. to 10 Mc.,  
0.005% Tolerance, \$5

★

10 Mc. to 18 Mc.,  
0.005% Tolerance, \$6

★

**Regrinds \$3**

THESE PRICES ARE SUBJECT  
TO SALES TAX

**SPECIAL CRYSTALS:  
PRICES  
ON APPLICATION**

## MAXWELL HOWDEN

15 CLAREMONT CRES.,  
CANTERBURY,  
VIC., 3126

Phone 83-5090

# LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages  
with more writing space.

Price 75c each

plus 17 Cents Post and Wrapping

Obtainable from your Divisional  
Secretary, or W.I.A., P.O. Box 38,  
East Melbourne, Vic., 3002



## TRIO TR2E 2 METRE TRANSCEIVER

- Triple conversion receiver with crystal locked 2nd and 3rd oscillators for maximum selectivity and sensitivity.
- Separate VFO tuning for both receiver and transmitter.
- Nuvostron RF amplifier.
- Provision for crystal locking of the transmitter.
- 12 volts DC (internal transistor power supply) and 230/240 volts AC operation.
- Noise limiter and squelch.
- 17 tubes, 4 transistors and 7 diodes.
- 1 microvolt sensitivity for 10 db. S/N ratio at 148 Mc.
- "S" meter, RF output meter, and "netting" control.

**Price: \$282.00**

## MILLER 8903B PRE-WIRED I.F. STRIPS

455 Kc. centre frequency, 55 db. gain, uses two PNP transistors and diode detector. Bandwidth 5 Kc. at 6 db. DC requirements: 6 volts at 2 mA.

**Price: \$9.70**

Plus pack and post 25 cents

## VALVE SPECIALS

ATS25 ceramic base 807, 70c or three for \$2.

815, 70c.

6AC7, 20c or 12 for \$2.

6J6, 30c or 7 for \$2.

6CQ6, 20c or 6 for \$1.

VR150/30, 75c or 3 for \$2.

QB2/250 (813), new and boxed, \$7 ea.

6H6 metal, 20c each.

DM71 indicator tube, 40c ea. or 6 for \$2.

6F33, 30c ea.

## RESISTORS

Mixed Values

\$2 per 100

plus postage 20 cents

## CAPACITORS

Mixed Values

80 for \$2

plus postage 20 cents

## STAR ST-700 TRANSMITTER

**SSB — AM — CW**

**80 Metres to 10 Metres**

- Ultra-precision three-stage double gear tuning mechanism, completely free of backlash, spreads each 600 Kc. over 1.68 metres with 1 Kc. dial calibrations.
- Stability better than 100 cycles. "Vackar" type VFO. Voltage regulated power supply.
- Specially designed filter at 455 Kc. selectable upper or lower sideband. Carrier and sideband suppression 50 db. or more.
- May be connected with STAR SR-700A receiver for transceive operation.
- Fully adjustable VOX and ANTITRIP circuits for automatic transmission/reception.
- Press-to-talk relay, break-in keying and sidetone oscillator for CW monitoring.
- Automatic level control circuit assures high quality distortion free SSB.
- Built-in antenna relay.
- Final stage uses two 6146s in parallel with conservatively rated input of 250 watts PEP on SSB and CW, 100 watts on AM.
- Built-in heavy duty power supply with adequate reserve margin assures trouble-free operation.
- Power supply 220 to 240 volts AC 50 cycles.

**Price: \$519.50**

## CARBON POTS

**20 cents ea.**

## WIRE-WOUND POTS

**40 cents ea.**

## 3000 TYPE RELAYS

large range

**Only 50 cents ea.**

## VACUUM SEALED RELAYS

mainly 24 volts

**50 cents ea.**

## TRANSISTORISED COMPUTER BOARDS

from \$3

## FULL RANGE OF MULTIMETERS

## STAR SR-700A RECEIVER

**SSB — AM — CW**

- Ultra-precision three-stage double gear tuning mechanism, completely free of backlash, spreads each 600 Kc. over 1.68 metres with 1 Kc. dial calibration.
- Stability better than 100 cycles. "Vackar" type VFO. Voltage regulated power supply.
- Triple conversion, IF's 1650 Kc. and 55 Kc. First and third oscillators crystal controlled.
- Image ratio better than 60 db. on all bands. Beat interference below noise level.
- Variable selectivity band pass filter at 55 Kc. provides steep cut offs and a good shape factor. Four positions: 0.5, 1.2, 2.5 and 4 Kc. (at 6 db. down).
- T-notch filter provides better than 50 db. attenuation.
- Variable decay AGC. Variable BFO tuning.
- Output terminal on VFO for transceive operation.
- Product detector for SSB/CW. Diode detector for AM.
- Noise limiter with adjustable clipping level operates on AM, SSB and CW.
- Built-in 100 Kc. crystal calibrator (crystal included). Zero adjustment on VFO.
- Sensitivity better than 0.5  $\mu$ V. for 10 db. S + N ratio on SSB and CW, better than 1  $\mu$ V. on AM.
- Power output, 1 watt. Impedance, 4 ohms.
- 13 tubes, 6 diodes.

**Price: \$461.50**

## MARCONI TF885A VIDEO OSCILLATOR

**Price: \$120**

## SANSEI SE405 S.W.R. BRIDGE

1 Mc. to 150 Mc., also doubles as a Field Strength Meter

**Price: \$21 inc. tax**

## WE SPECIALISE IN CRO's

Cossor, Solarton, Dumont, A.W.A., Philips, E.M.I.

**From \$80**

See us for all Marconi Test Equipment

*All Prices Subject to Alteration without Notice. All Items Freight Extra.*

# UNITED TRADE SALES PTY. LTD.

280 LONSDALE ST., MELBOURNE, VIC. (Opp. Myers)

Phone 663-3815

# Modern SSB by Yaesu!



## TRANSCIVER MODEL FTDX-400

Latest version with all improvements including double knob dual ratio VFO tuning control. Also has provision for power take-off and connections to enable use of FTV-650 six metre transverter.

### COMPARE THE FEATURES:

- ★ Five bands, including full coverage on 10 metres.
- ★ A powerful 400 watts (500 watts speech peak SSB input).
- ★ Power Supply built in, 230v, 50 cycles AC (no extra charge!).
- ★ Selectable USB/LSB, CW and AM, normal or break-in keying.
- ★ Carrier input adjustable for safe tune up.
- ★ PA uses pair of new heavy duty pentodes, type 6X06, 33 watt plate dissipation.
- ★ VOX is included, as well as PTT and panel control.
- ★ 100 kc. and 25 kc. dual calibrator.
- ★ Sidetone CW monitor.
- ★ Multi-scale panel meter, fully calibrated, provides direct reading of PA current, plus relative power output, ALC indication, Rx "S" units.
- ★ Offset tuning, plus or minus 5 kc. is provided by clarifier control, which is selectable CW, Rx, Rx and Tx.
- ★ VFO dial readout of 1 kc.
- ★ Dial forward reading all bands.
- ★ Provision for external VFO for split frequency operation, plus built-in four crystal locked channel facility.
- ★ Receiver sensitivity better than 0.5 uV, S/N 20 db.
- ★ Fast and slow selectable receiver AGC.
- ★ All plugs, circuit and instruction manual provided.
- ★ PTT microphone included—free.
- ★ Superbly neat construction, very accessible for servicing.
- ★ Solid, charcoal blue cabinet with lift-off lid, 12 3/4 x 8 1/4 x 13 1/4 inches. Matt finish aluminium panel.
- ★ 18 valves, 9 transistors and 33 diodes.

As the authorised Australian Agent for YAESU, it is our responsibility to provide factory-backed warranty, with spares and service availability. Write for illustrated brochure with circuit, specifications and revised prices.

### FOR PRESTIGE PERFORMANCE — CHOOSE YAESU

Also available: Matching speakers, Hy-Gain antennas, Kyoritsu SWR meters, co-ax. connectors, LP filters, spares, including valves, for Yaesu equipment, PTT microphones. Prices and specs. subject to changes.

Australian Agent:

## BAIL ELECTRONIC SERVICES

60 Shannon St., Box Hill North, Vic., 3129. Phone 89-2213

Rep. in N.S.W.:

A. J. ("SANDY") BRUCESMITH

47 HYMAN ST., TAMWORTH, N.S.W., 2340

Phone (STD 067) 66-1010